

CSE 112: Computer Organization

Instructor: Sujay Deb

Lecture 19



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI




Pipelined Processor Control Hazards

Control Hazards

- **beq:**
 - Branch **not determined until the Execute stage** of pipeline
 - **Instructions** after branch **fetch** before branch occurs
 - These **2 instructions must be flushed** if branch happens

Control Hazards

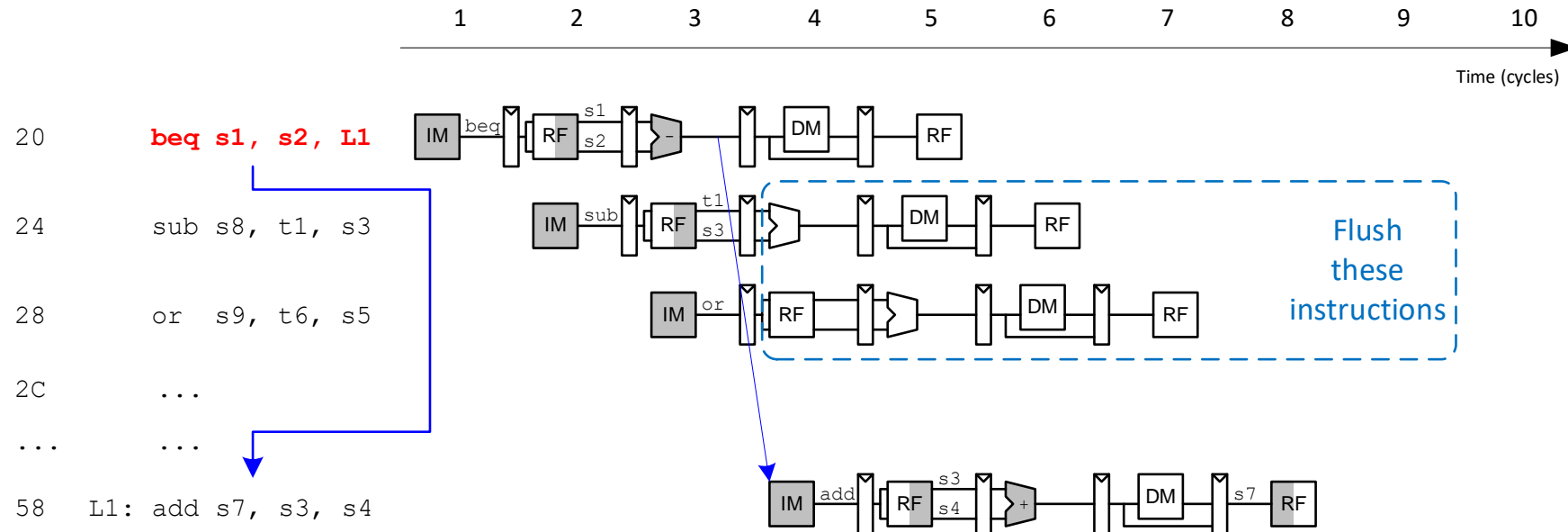

Branch misprediction penalty:

The number of instructions flushed when a branch is taken (in this case, 2 instructions)


Control Hazards: Flushing Logic

- If branch is taken in execute stage, need to flush the instructions in the Fetch and Decode stages
 - Do this by clearing Decode and Execute Pipeline registers using *FlushD* and *FlushE*
- **Equations:**


$$FlushD = PCSrcE$$

$$FlushE = lwStall \text{ OR } PCSrcE$$

Control Hazards: Flushing Hardware

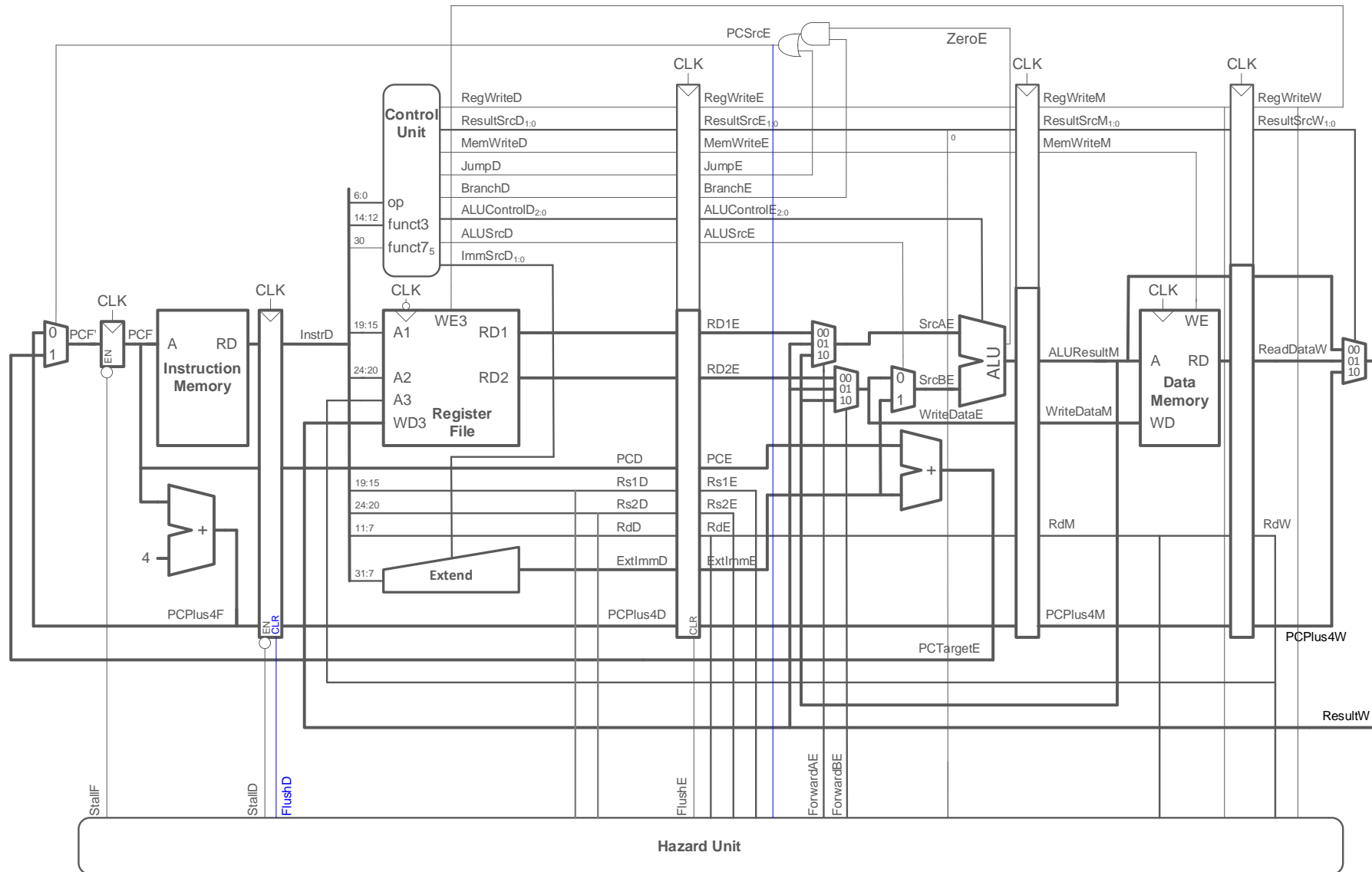

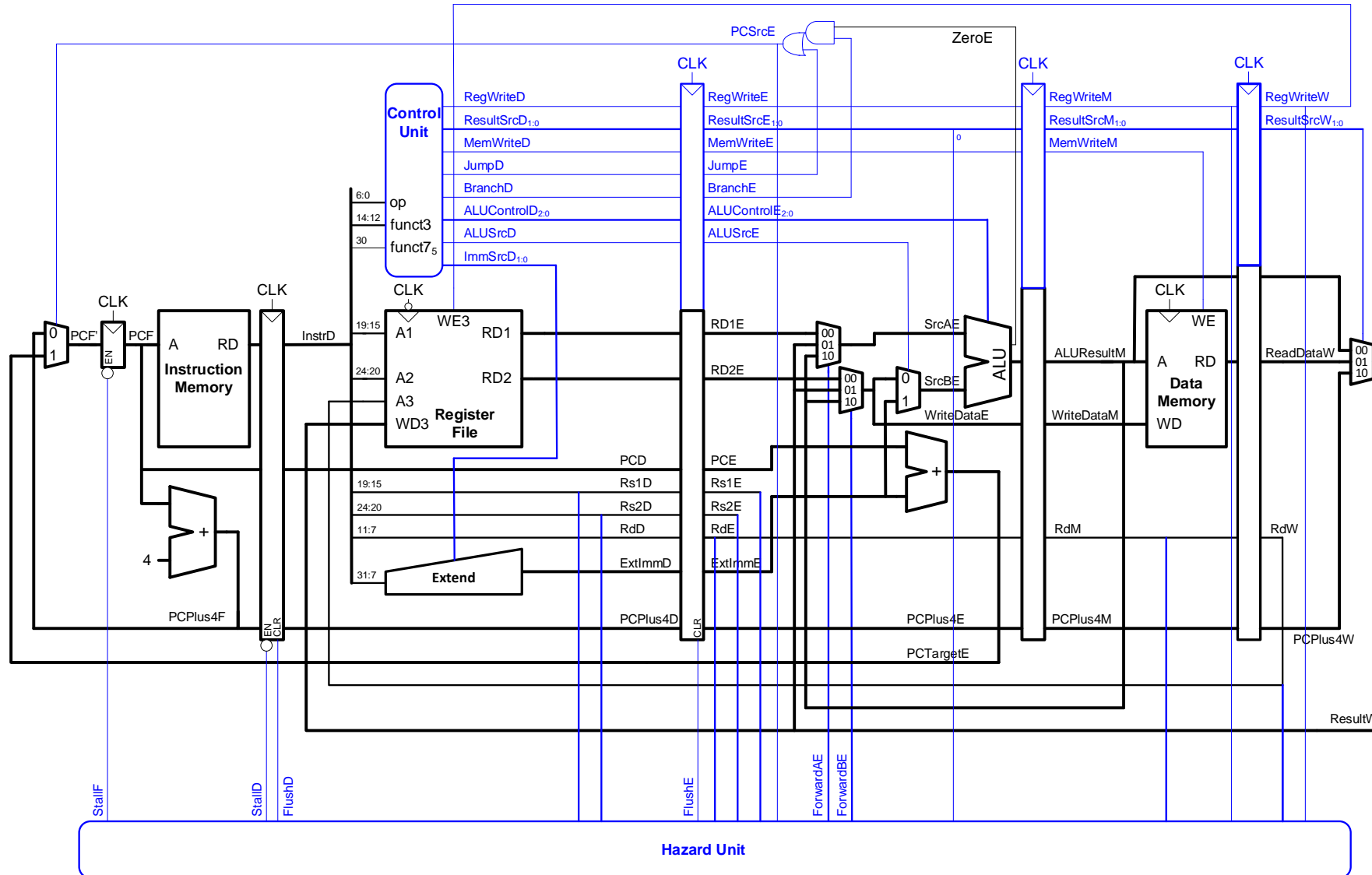RISC-V Pipelined Processor with Hazard Unit



Summary of Hazard Logic

Data hazard logic (shown for SrcA of ALU):

```
if      ((Rs1E == RdM) AND RegWriteM) AND (Rs1E != 0)    // Case 1
        ForwardAE = 10
else if ((Rs1E == RdW) AND RegWriteW) AND (Rs1E != 0)    // Case 2
        ForwardAE = 01
else    ForwardAE = 00                                     // Case 3
```

Load word stall logic:

```
lwStall = ((Rs1D == RdE) OR (Rs2D == RdE)) AND ResultSrcE0
StallF = StallD = lwStall
```

Control hazard flush:

```
FlushD = PCSrcE
FlushE = lwStall OR PCSrcE
```


Class Interaction # 21



Pipelined Performance

Pipelined Processor Performance Example

- **SPECINT2000 benchmark:**
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type
- **Suppose:**
 - 40% of loads used by next instruction
 - 50% of branches mispredicted
- **What is the average CPI?** (Ideally it's 1, but...)

Pipelined Processor Performance Example


Pipelined processor critical path:

$$T_{c_pipelined} = \max \text{ of}$$

$t_{pcq} + t_{mem} + t_{setup}$	Fetch
$2(t_{RFread} + t_{setup})$	Decode
$t_{pcq} + 4t_{mux} + t_{ALU} + t_{AND-OR} + t_{setup}$	Execute
$t_{pcq} + t_{mem} + t_{setup}$	Memory
$2(t_{pcq} + t_{mux} + t_{RFwrite})$	Writeback

- Decode and Writeback stages **both use the register file** in each cycle
- So each stage gets half of the cycle time ($T_c/2$) to do their work
- Or, stated a different way, **2x of their work** must fit in a cycle (T_c)

Pipelined Critical Path: Execute Stage

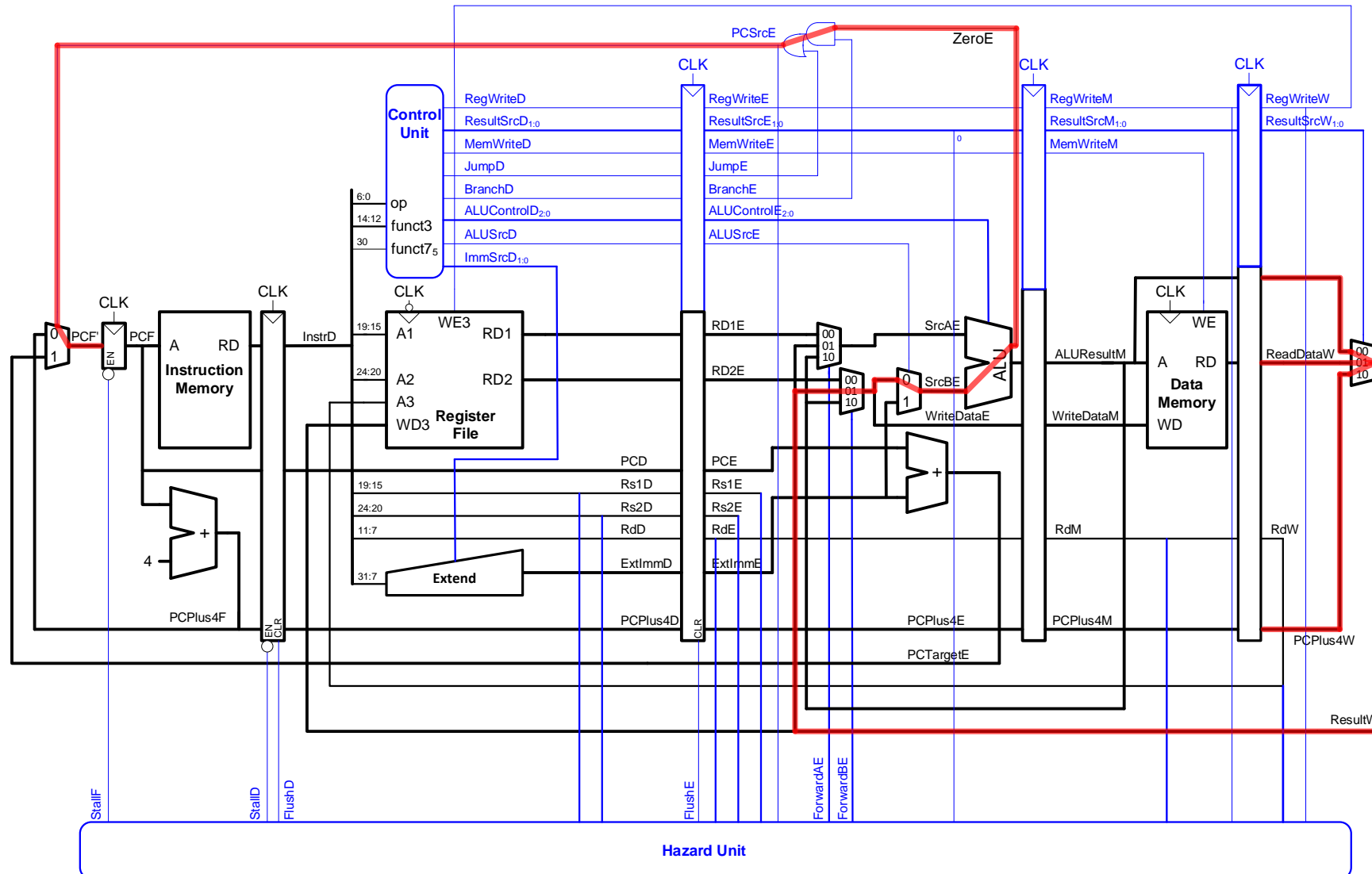

Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (Control Unit)	t_{dec}	25
Extend unit	t_{dec}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{c_pipelined} = t_{pcq} + 4t_{mux} + t_{ALU} + t_{AND-OR} + t_{setup}$$

$$=$$

Pipelined Performance Example

Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1.23)(350 \times 10^{-12}) \\ &= \text{43 seconds}\end{aligned}$$

Processor Performance Comparison

Processor	Execution Time (seconds)	Speedup (single-cycle as baseline)
Single-cycle	75	1
Pipelined	43	1.7

Class Interaction # 22

