

ECE113: Basic Electronics (BE)

Winter 2025

Mid Semester Exam

Date: 27-Feb-2025

Duration: 2 Hours

Total Marks: 40

[CO1, CO2] **Q1: [10 Marks]** Find the value of V_x and V_y by using Superposition theorem (in Figure-1).

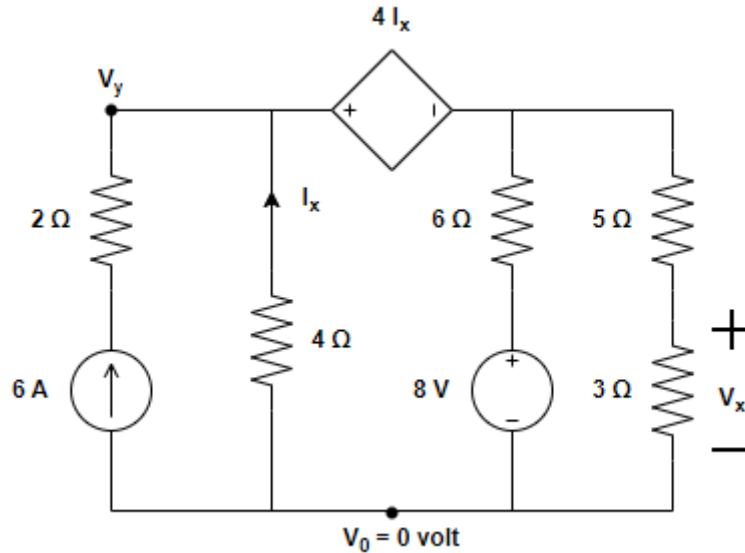


Figure 1

[CO3] **Q2: [10 Marks]** In the circuit shown (in Figure-2) at time $t = 0 \text{ sec}$ the switch (S) is connected to position-A. After one time constant ($T=2 \text{ sec}$) the switch (S) is transferred to position-B. Find-

- (a) Voltage response across capacitor, when the switch is connected to position-A
- (b) Current response through capacitor, when the switch is connected to position-B.

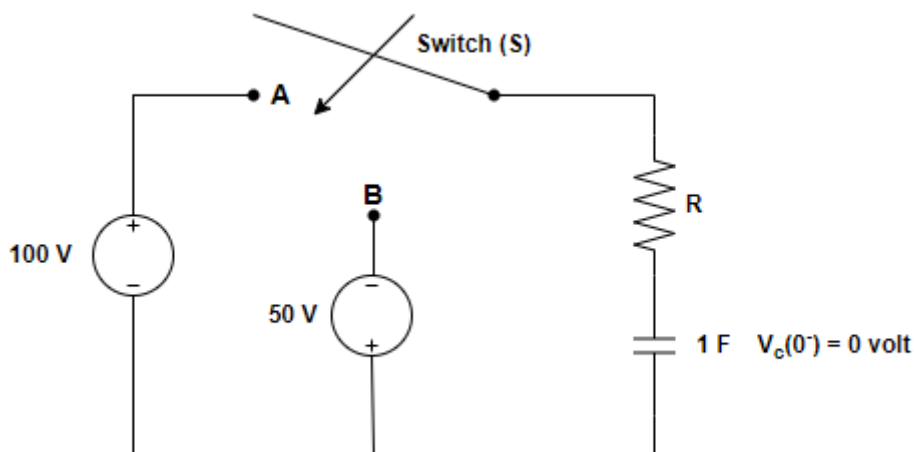


Figure 2

[CO3] **Q3: [10 Marks]** In Figure-3, find-

- (a) $i_1(0^+)$
- (b) $i_2(0^+)$
- (c) $V_c(0^+)$
- (d) $\frac{di_1(0^+)}{dt}$
- (e) $\frac{di_2(0^+)}{dt}$
- (f) $\frac{d^2 i_1(0^+)}{dt^2}$
- (g) $\frac{d^2 i_2(0^+)}{dt^2}$

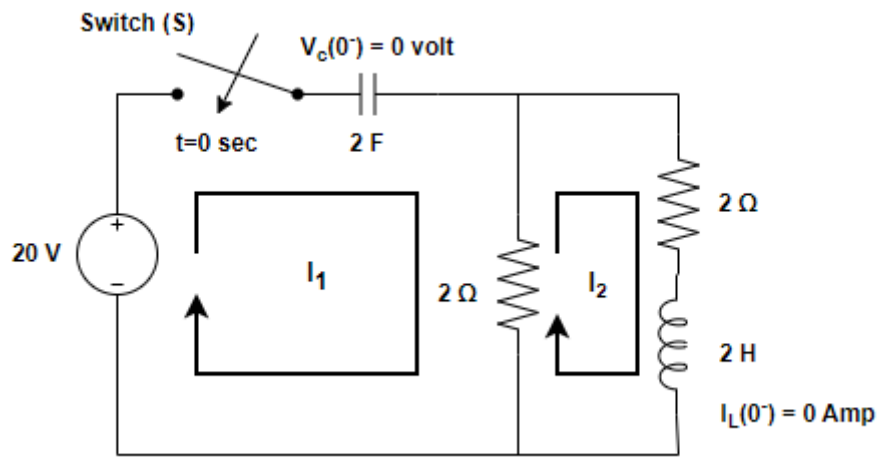


Figure 3

[CO1, CO2] Q4: [5 Marks] Find the value of current (I_0) (in Figure-4).

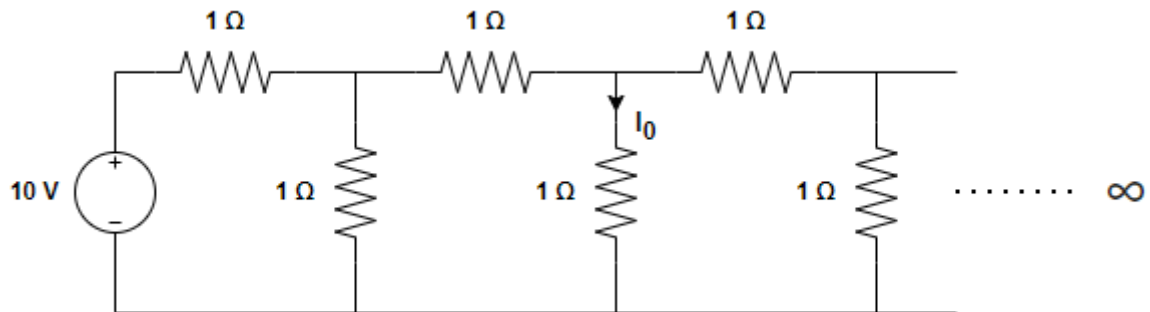


Figure 4

[CO1, CO2] Q5: [5 Marks] Find the value of resistance "R" to obtain maximum power transfer from Network-A to Network-B (in Figure-5) at steady state.

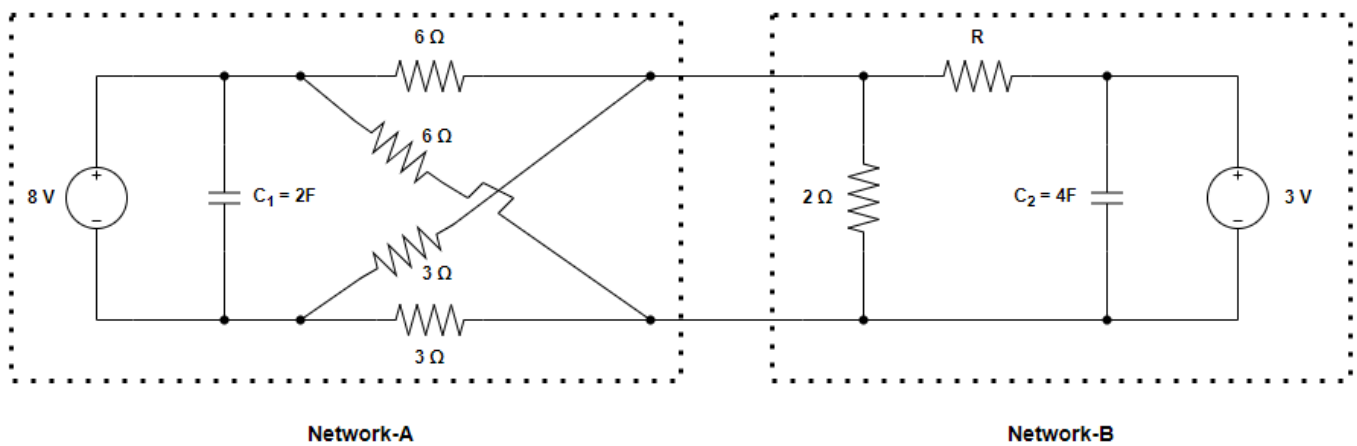


Figure 5