

Tutorial-2

Winter_2025

Basic Electronics (ECE113)

Q1: Transform the dependent source to a voltage source, in the given following circuit of Figure-1 using source transformation then calculate V_0 .

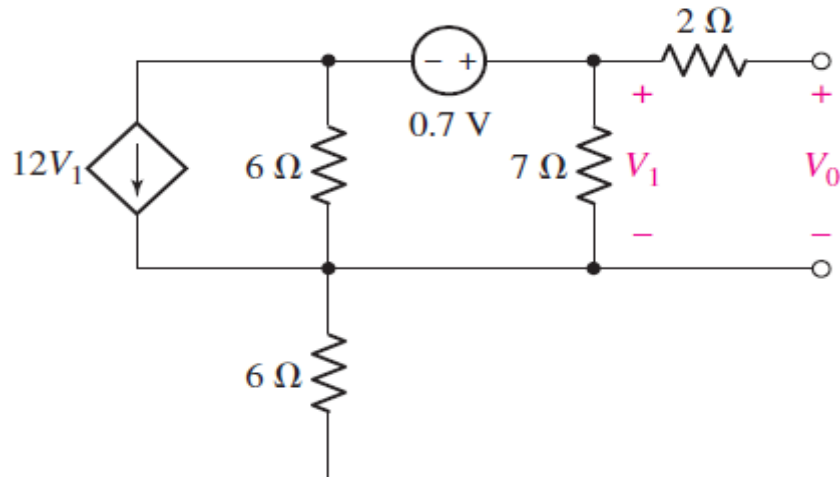


Figure 1

Q2: Employ Thevenin's theorem to obtain a two-component equivalent for the network shown in Figure-2 & Determine the power supplied to a $1 \text{ M } \Omega$ resistor connected to the network if current $I_1 = 19 \text{ } \mu\text{A}$, $R_1 = R_2 = 1.6 \text{ M } \Omega$, $R_3 = 3 \text{ M } \Omega$, and $R_4 = R_5 = 1.2 \text{ M } \Omega$.

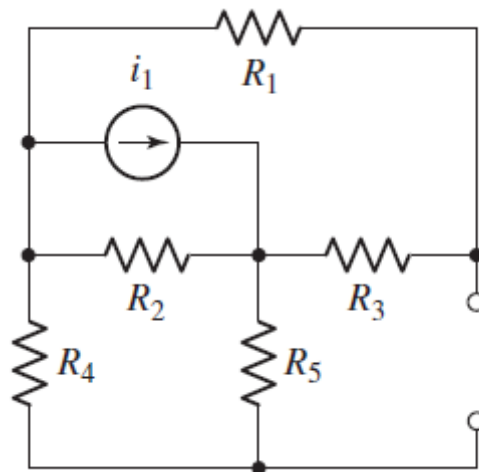


Figure 2

Q3: With regard to the network depicted in Figure-3, determine the Thevenin equivalent as seen by an element connected to terminals- (i) *a and b* (ii) *a and c* (iii) *b and c*.

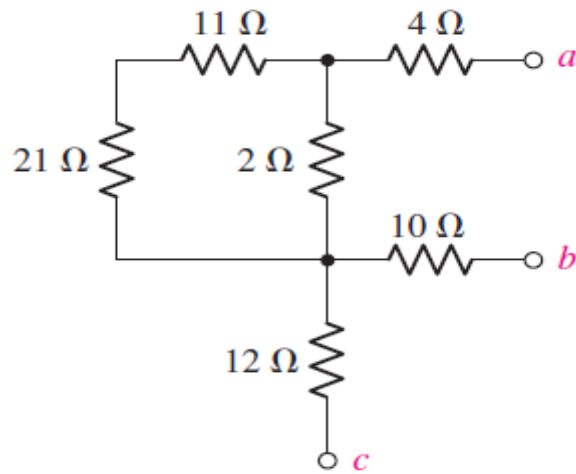


Figure 3

Q4: For the circuit of Figure-4, **(a)** Employ Norton's theorem to reduce the network connected to R_L to only two components. **(b)** Calculate the downward directed current flowing through R_L if it is a $3.3 \text{ k}\Omega$ resistor.

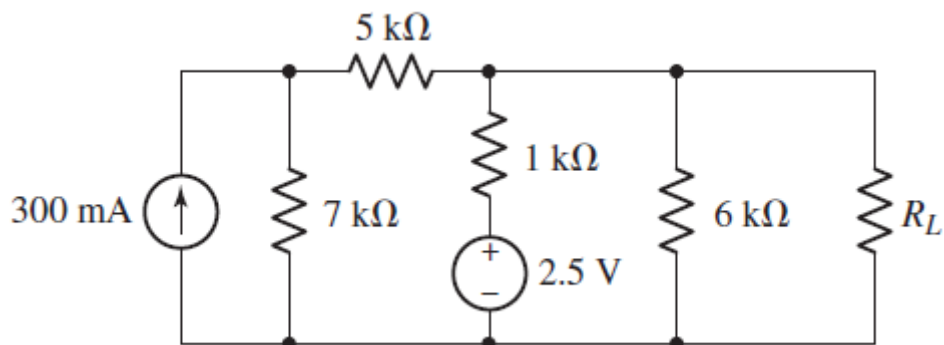


Figure 4

Q5: Determine the Thevenin equivalent of the network shown in Figure-5, as seen looking into the two open terminals.

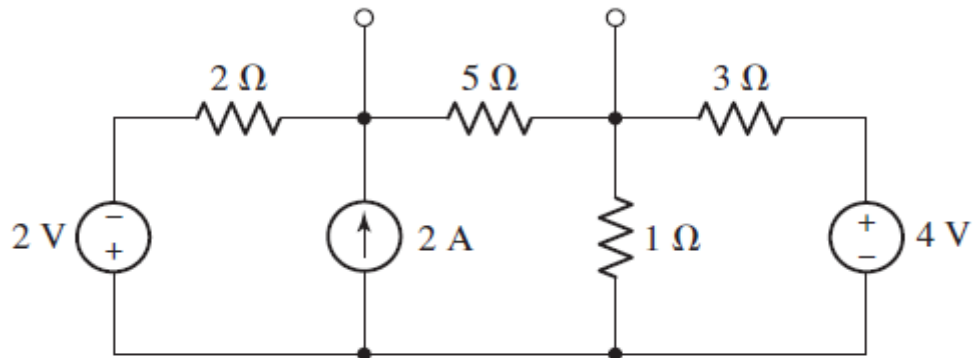


Figure 5

Q6: With regard to the circuit represented in Figure-6, first transform both voltage sources to current sources, reduce the number of elements as much as possible, and determine the voltage V_3 .

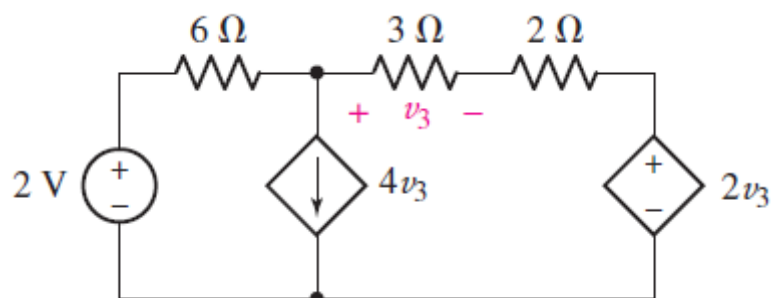


Figure 6

Q7: For the circuit of Figure-7, plot i_L versus v_L corresponding to the range of $0 \leq R \leq \infty$.

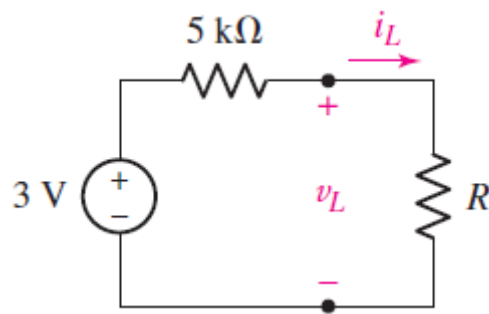


Figure 7

Q8: (a) Employ superposition to determine the individual contribution from each independent source to the voltage v as labelled in the circuit shown in Figure-8. **(b)** Compute the power absorbed by the 2Ω resistor.

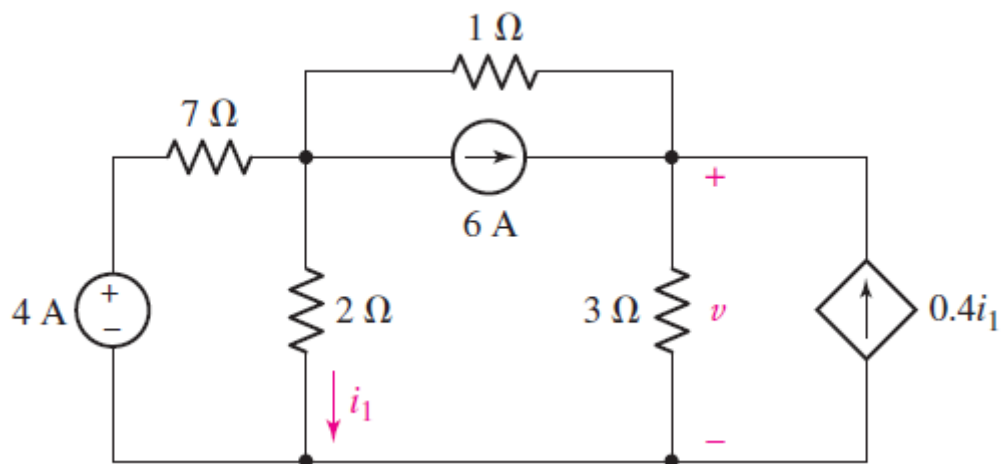


Figure 8