

Digital Circuits (2024) - Tutorial Five

Question 1: Given the equation $c = a \cdot b$, determine what the variable c represents.

Question 2: Given the equation $c = a \cdot b + a \cdot \bar{b}$, determine what the variable c represents.

Question 3: Consider a system with three inputs (**a**, **b**, **c**) and one output (**d**). The output produces a logical one when:

- Input **a** is logical one, or
- Inputs **b** and **c** are both logical one.

Sketch the circuit that represents the system and write an equation to represent the output in terms of the inputs.

Question 4: Consider a system with three inputs (**a**, **b**, **c**) and one output (**d**). The relationship between inputs and output is given as:

a	b	c	d
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

- Write the sum of products equation to represent the output in terms of the inputs.
- Reduce the number of terms in the equation.
- Sketch a circuit that emulates the system.

Question 5: Consider a system represented by an unknown circuit labeled **e**. Write a truth table to represent the relationship between the inputs and the output of the system.

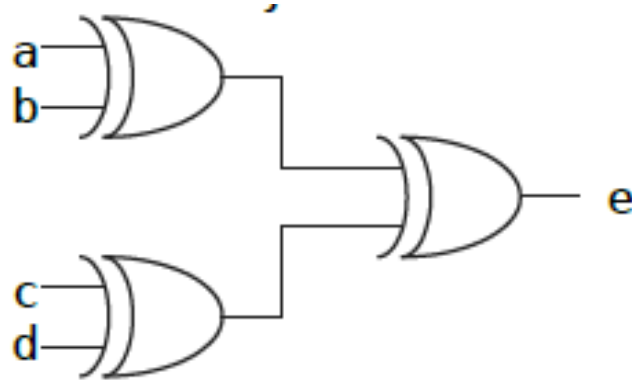


Figure 1: Question 5

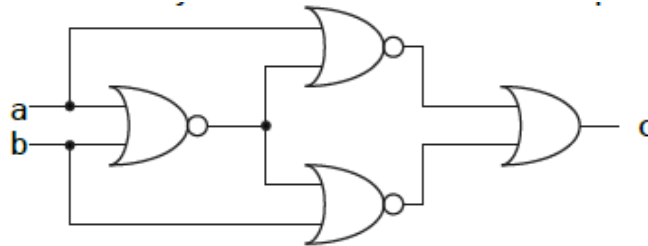


Figure 2: Question 6

Question 6: Consider a system represented by an unknown circuit labeled c . Write an equation and a truth table to represent the relationship between the inputs and the output of the system.

Question 7: Given the following truth table:

a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

Is the following equation correct? Justify your answer:

$$a \cdot \bar{b} + \bar{a} \cdot b = a \oplus b$$