

# CSE 112: Computer Organization

---

Instructor: Sujay Deb

## Lecture 12



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI



# **Single-Cycle RISC-V Processor**

# Example Program


- Design datapath
- View example program executing

## Example Program:

Address	Instruction	Type	Fields					Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm <sub>11:0</sub>	rs1	f3	rd	op	0000011	FFC4A303
0x1004	sw x6, 8(x9)	S	imm <sub>11:5</sub>	rs2	rs1	f3	imm <sub>4:0</sub>	op	0100011 0064A423
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	0110011 0062E233
0x100C	beq x4, x4, L7	B	imm <sub>12,10:5</sub>	rs2	rs1	f3	imm <sub>4:1,11</sub>	op	1100011 FE420AE3

# Single-Cycle Datapath: PC Increment
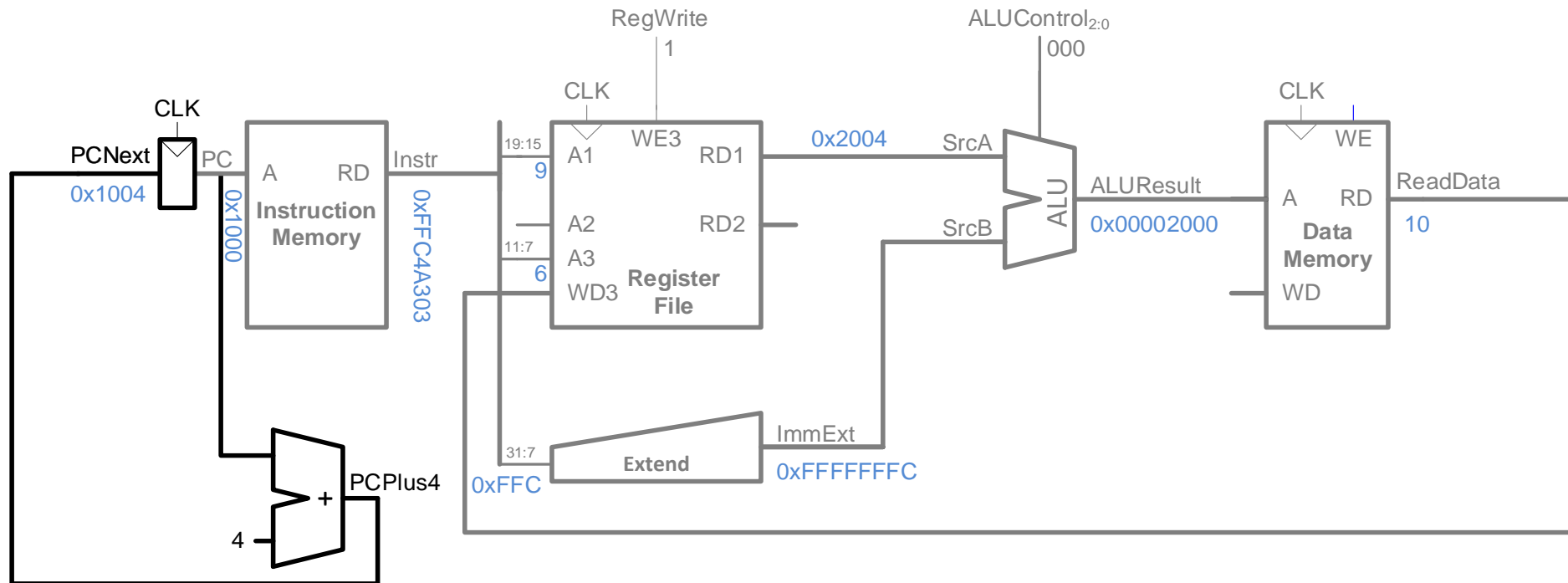
## STEP 6: Determine address of next instruction




Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	<div><div>imm<sub>11:0</sub></div><div>111111111100</div><div>rs1</div><div>01001</div><div>f3</div><div>010</div><div>rd</div><div>00110</div><div>op</div><div>0000011</div></div>	FFC4A303

# **Single-Cycle Datapath: Other Instructions**
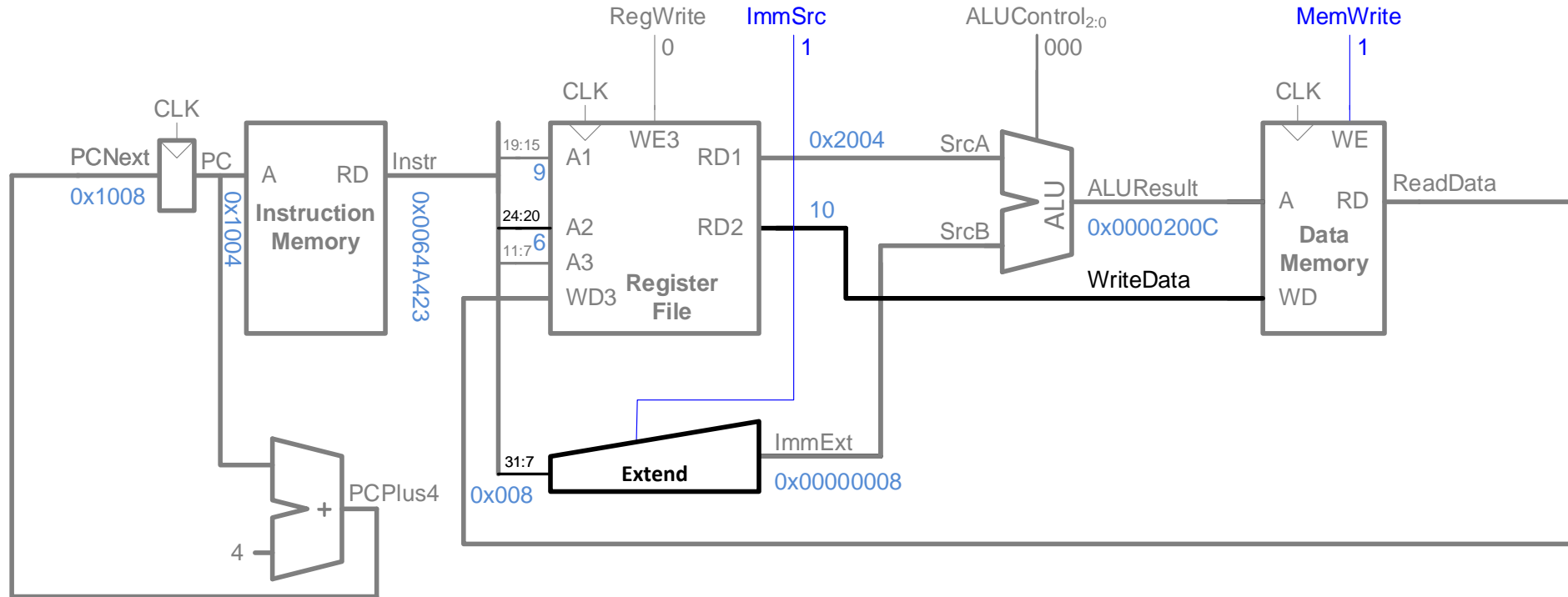
# Single-Cycle Datapath: sw

- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite




Address	Instruction	Type	Fields					Machine Language	
			imm <sub>11:5</sub>	rs2	rs1	f3	imm <sub>4:0</sub>	op	
0x1004	sw x6, 8(x9)	S	00000000	00110	01001	010	01000	0100011	0064A423


# Single-Cycle Datapath: Immediate

ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, <b>instr[31:20]</b> }	I-Type
1	{{20{instr[31]}}, <b>instr[31:25], instr[11:7]</b> }	S-Type

## I-Type

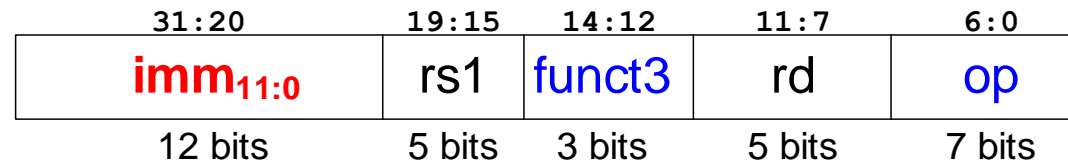


## S-Type

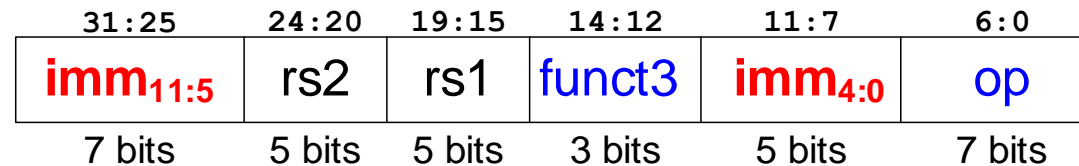
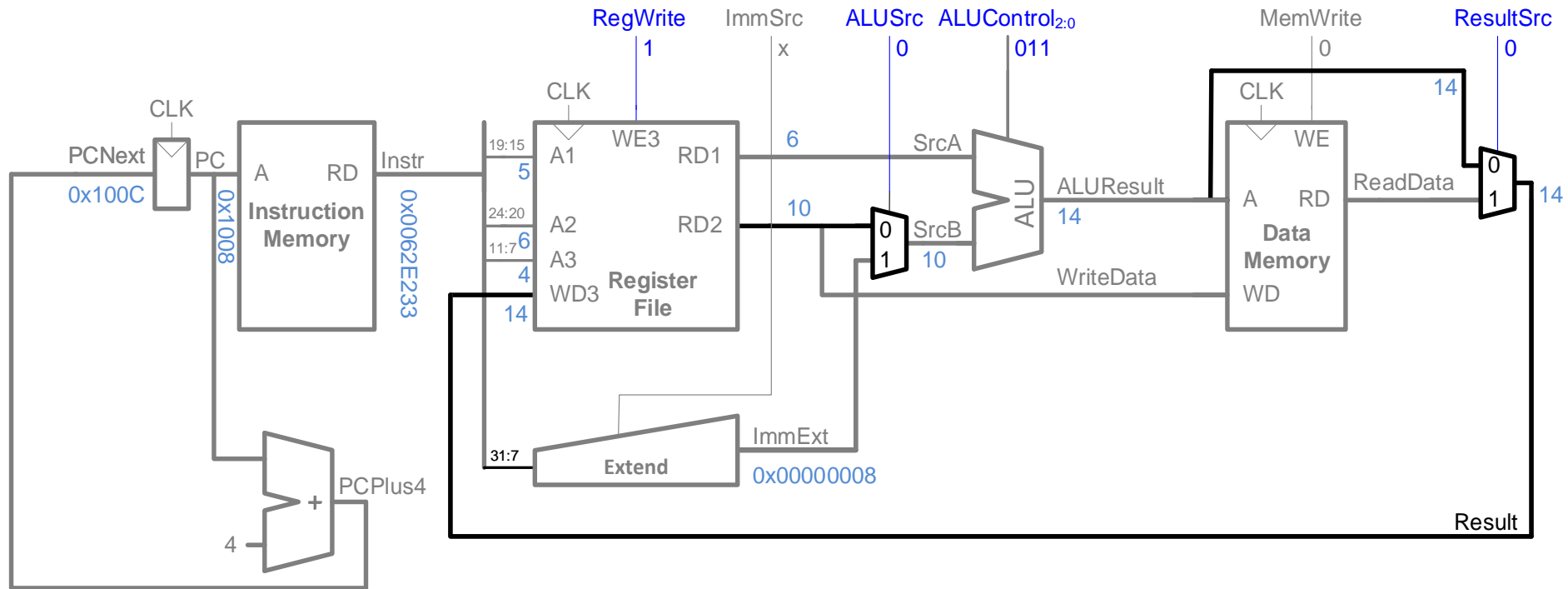
# Single-Cycle Datapath: R-type

- Read from **rs1** and **rs2** (instead of imm)
- Write *ALUResult* to **rd**




Address	Instruction	Type	Fields					Machine Language	
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	0062E233
			0000000	00110	00101	110	00100	0110011	


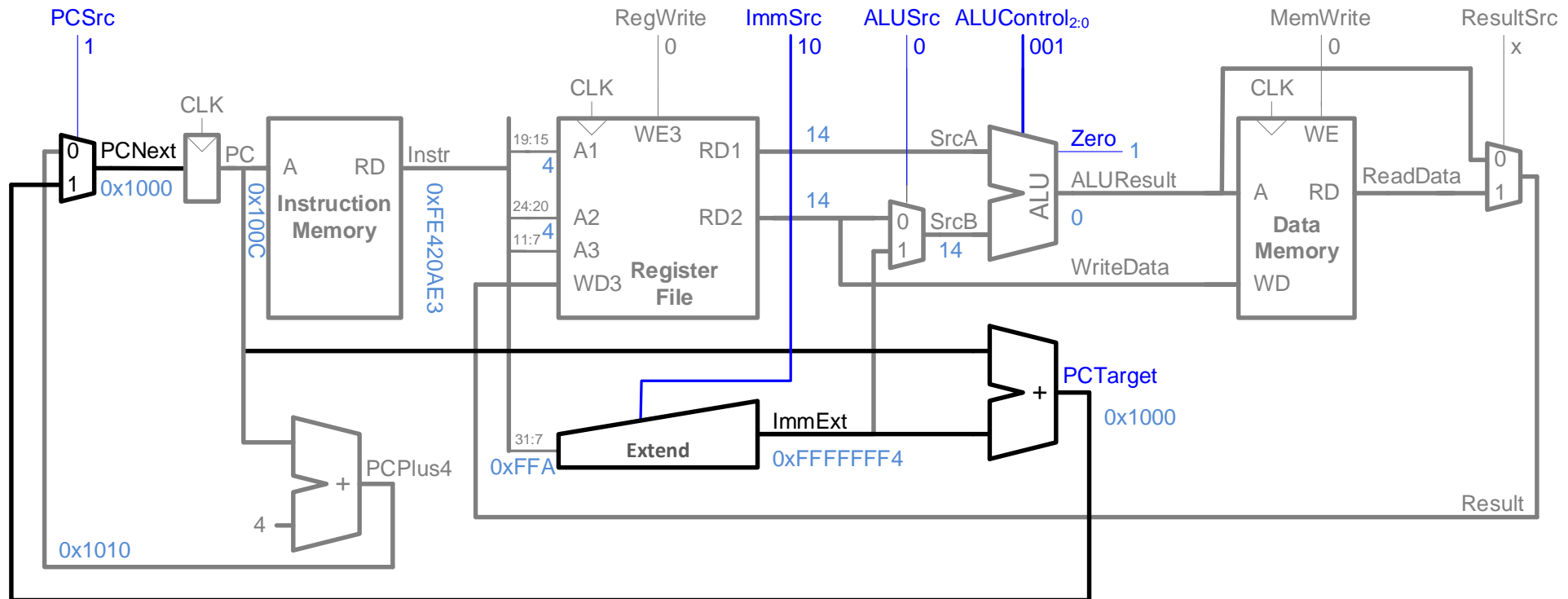
# Single-Cycle Datapath: beq

Calculate **target address**:  $PCTarget = PC + imm$




Address	Instruction	Type	Fields					Machine Language
0x100C	beq x4, x4, L7	B	$imm_{12,10:5}$	$rs2$	$rs1$	$f3$	$imm_{4:1,11}$	$op$
			1111111	00100	00100	000	10101	1100011
								FE420AE3


# Single-Cycle Datapath: ImmExt

ImmSrc <sub>1:0</sub>	ImmExt	Instruction Type
00	{{20{instr[31]}}, <b>instr[31:20]</b> }	I-Type
01	{{20{instr[31]}}, <b>instr[31:25], instr[11:7]</b> }	S-Type
10	{{19{instr[31]}}, <b>instr[31], instr[7], instr[30:25], instr[11:8], 1'b0</b> }	B-Type


## I-Type

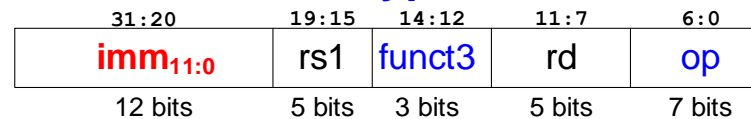


## S-Type

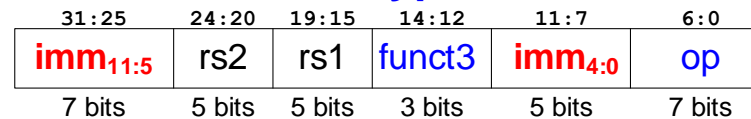

## B-Type

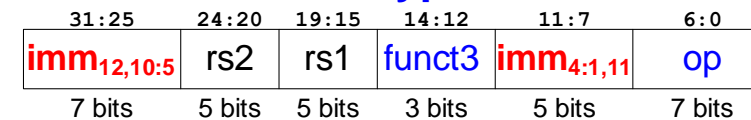


# Single-Cycle RISC-V Processor

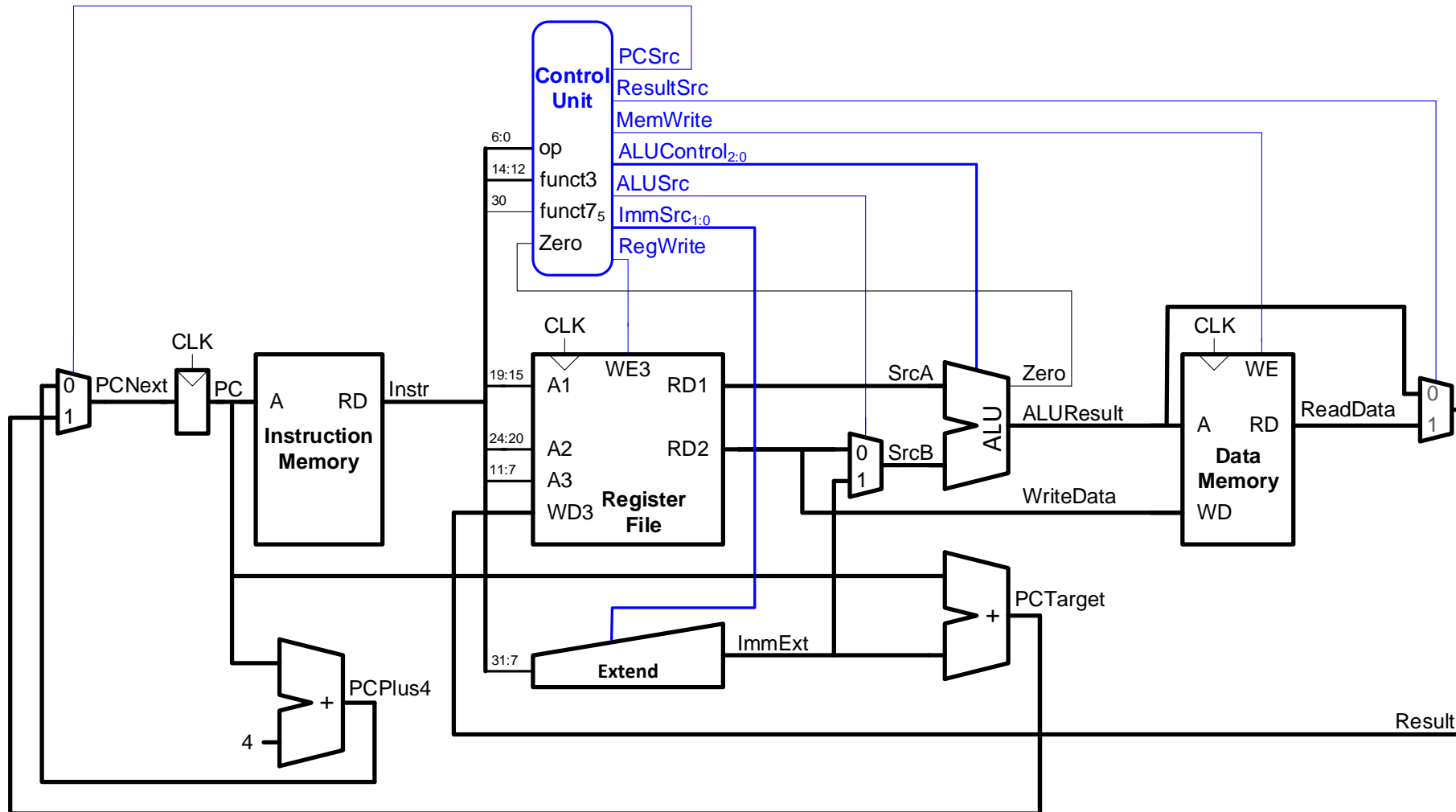


# **Single-Cycle Control**

# Single-Cycle Control

## High-Level View

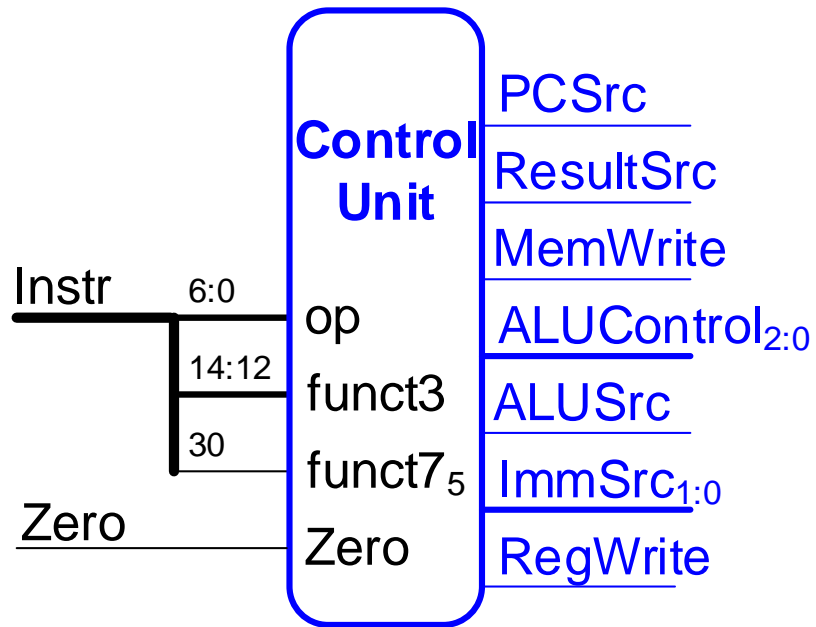


## Low-Level View

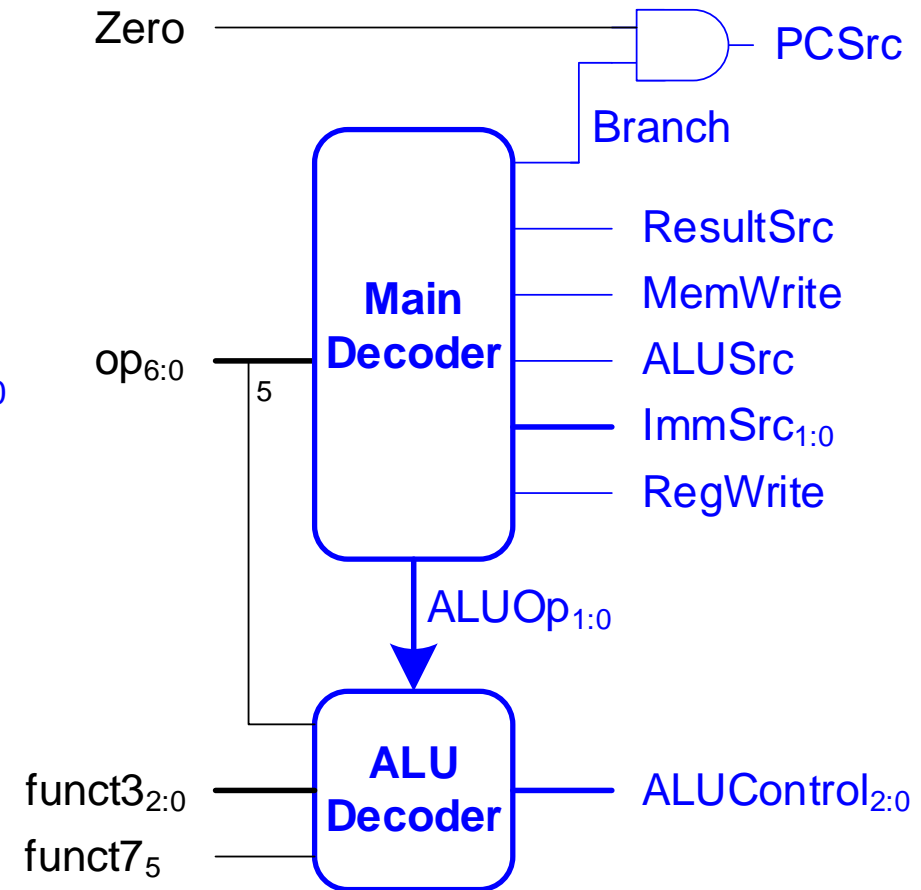


# Single-Cycle Control: Main Decoder

op	Instr.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	<b>lw</b>							
35	<b>sw</b>							
51	R-type							
99	<b>beq</b>							

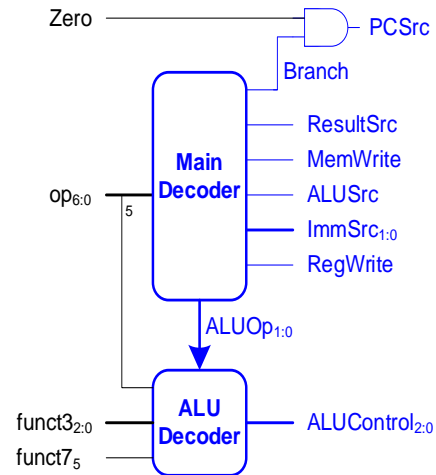


# Review: ALU

ALUControl <sub>2:0</sub>	Function
000	add
001	subtract
010	and
011	or
101	SLT

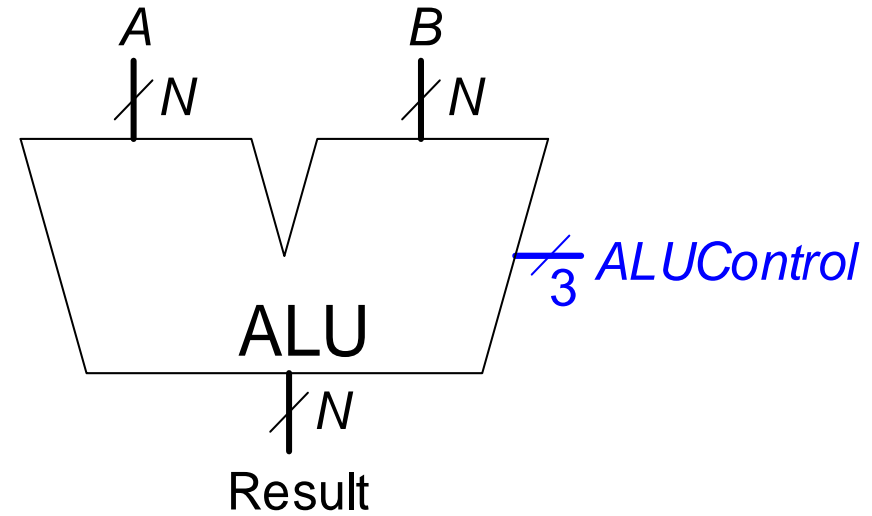


# Review: ALU

ALUControl <sub>2:0</sub>	Function
000	add
001	subtract
010	and
011	or
101	SLT

 




# Single-Cycle Control: ALU Decoder

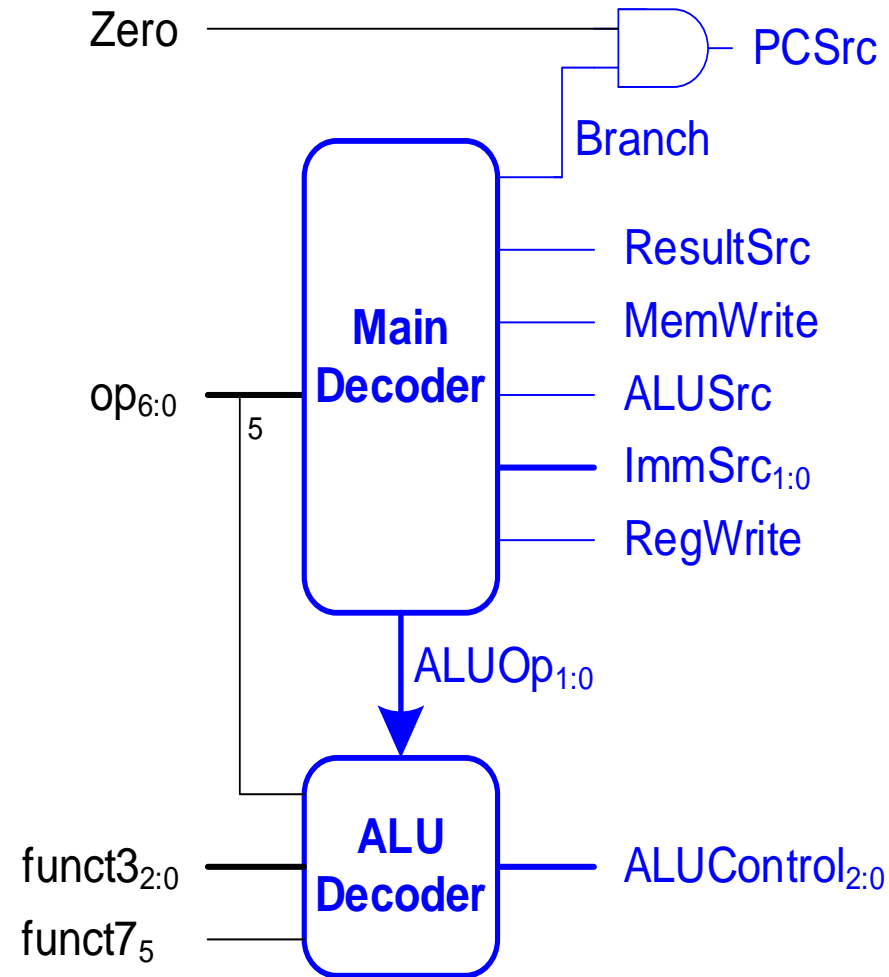


# Single-Cycle Control: ALU Decoder

<i>ALUOp</i>	funct3	op <sub>5</sub> , funct7 <sub>5</sub>	Instruction	<i>ALUControl</i> <sub>2:0</sub>
00	x	x	<b>lw, sw</b>	000 (add)
01	x	x	<b>beq</b>	001 (subtract)
10	000	00, 01, 10	<b>add</b>	000 (add)
	000	11	<b>sub</b>	001 (subtract)
	010	x	<b>slt</b>	101 (set less than)
	110	x	<b>or</b>	011 (or)
	111	x	<b>and</b>	010 (and)

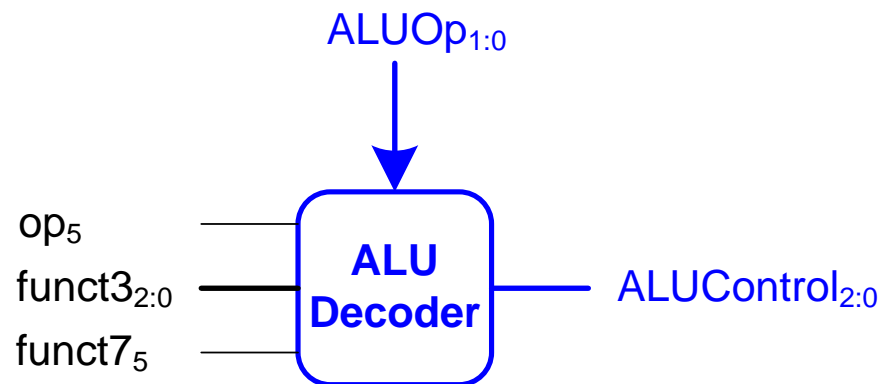

# Example: and

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

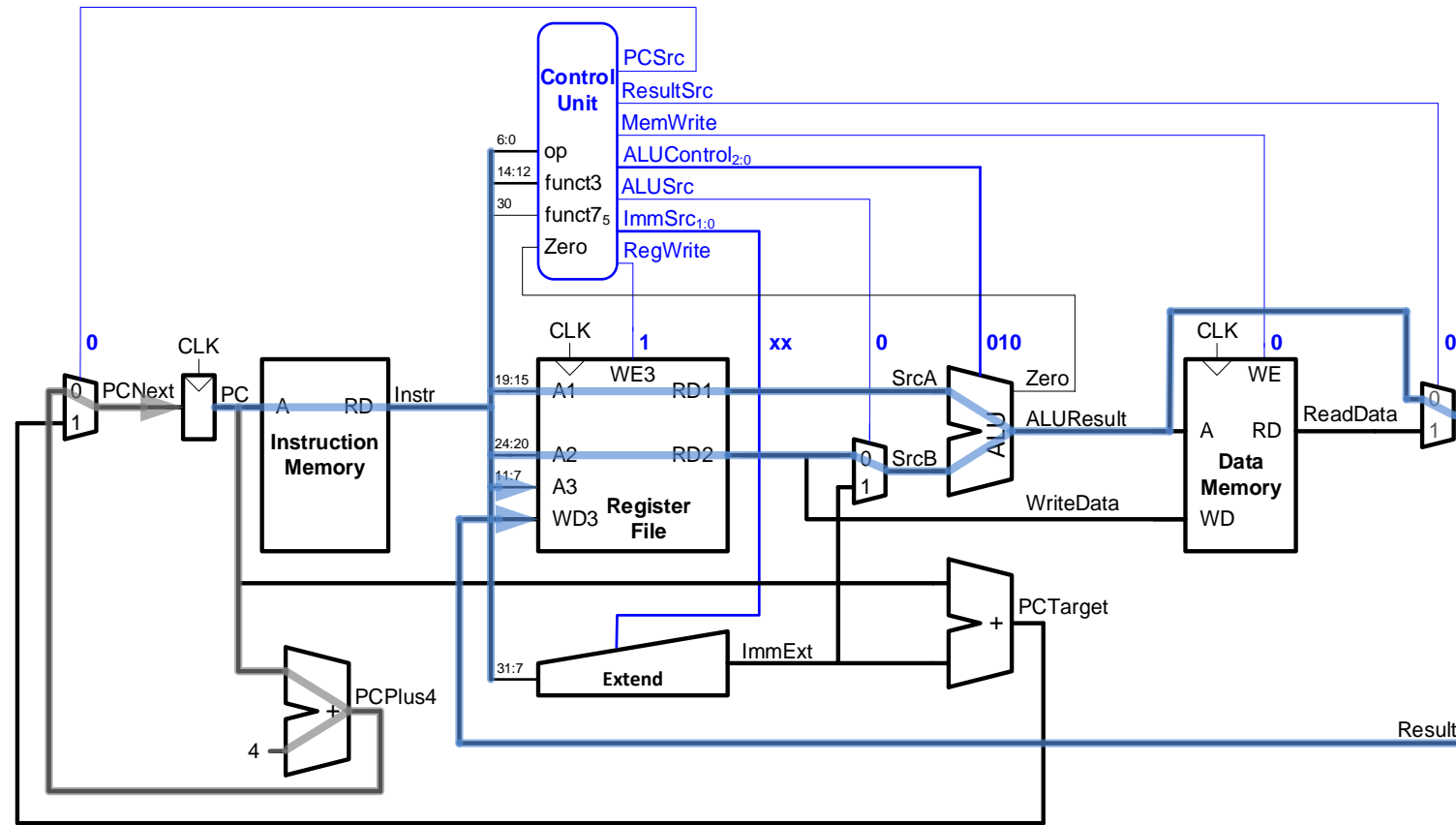

and x5, x6, x7

# **Extending the Single-Cycle Processor**

# Extended Functionality: I-Type ALU

Enhance the single-cycle processor to handle **I-Type ALU instructions**: `addi`, `andi`, `ori`, and `slti`


- **Similar to R-type** instructions
- But **second source** comes from **immediate**
- Change ***ALUSrc*** to select the immediate
- And ***ImmSrc*** to pick the correct immediate

# Extended Functionality: I-Type ALU

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	<b>lw</b>	1	00	1	0	1	0	00
35	<b>sw</b>	0	01	1	1	X	0	00
51	R-type	1	XX	0	0	0	0	10
99	<b>beq</b>	0	10	0	0	X	1	01
19	<b>I-type</b>	1	00	1	0	0	0	10

# Extended Functionality: addi

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	I-type	1	00	1	0	0	0	10

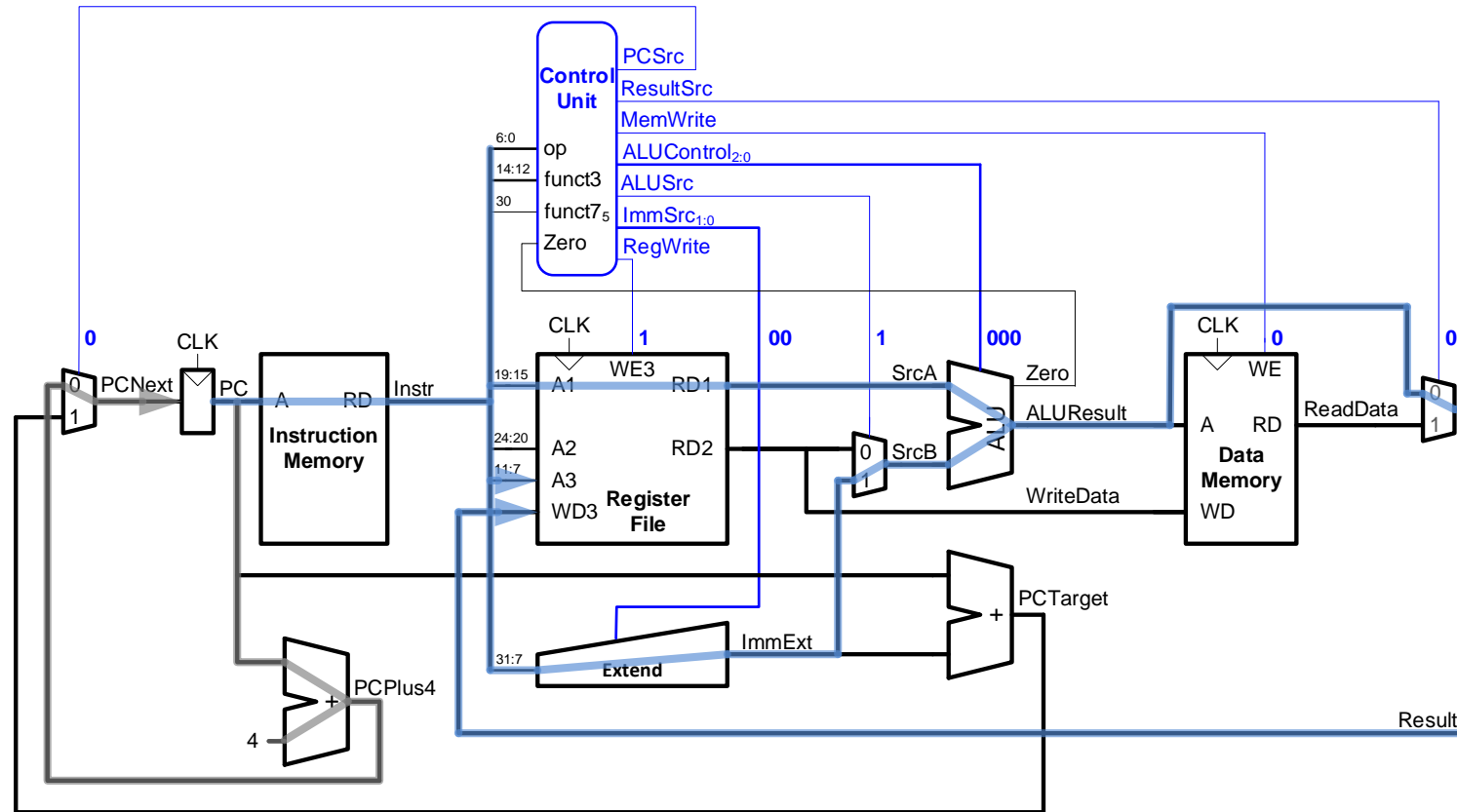

`addi x5, x6, -33`

## Class Interaction # 14

---

