

# Practice Sheet-3

## Winter\_2025

### Basic Electronics (ECE113)

---

**Q1:** In the given following circuit (Figure-1), the switch was initially closed to Position-1 for long time. At time  $t=0$  sec, the switch was transferred to Position-2, now find the value of voltage across capacitor at time  $t=0$  sec and  $t=160 \mu\text{sec}$ .

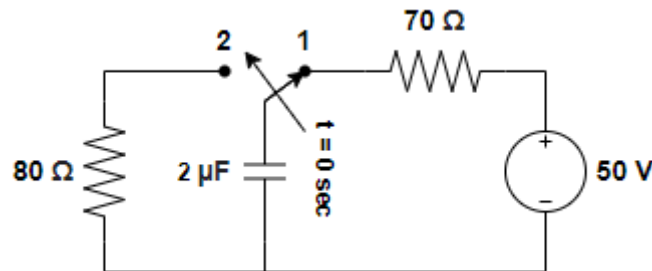


Figure 1

**Q2:** In the given following circuit (Figure-2), the switch was initially opened for a long time. The switch was closed at time  $t=0$  sec. Do-

- (a) Choose  $R_1$ , so that the response after  $t=0$  sec will be critically damped.
- (b) Choose  $R_2$ , so that  $V_C(0)=100$  Volt
- (c) Find  $V_C(t)$  at time  $t=1$  msec.

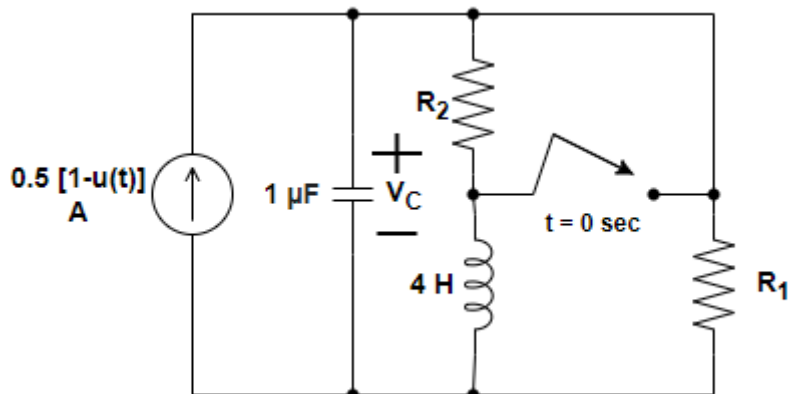


Figure 2

**Q3:** Find the value of  $I_C$  and  $I$  in the given following circuit (Figure-3).

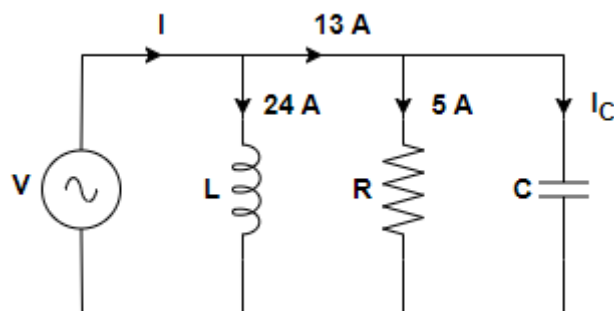


Figure 3

**Q4:** Find the value of current  $I_1$  and  $I_L$  in the circuit shown in Figure-4 for  $t > 0$  sec.

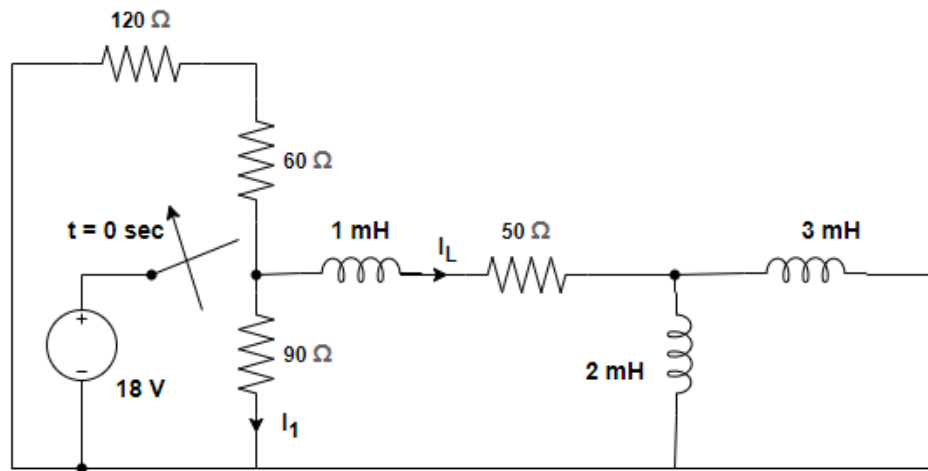


Figure 4

**Q5:** In the given following circuit (Figure-5), the switch was initially opened for a long time. The switch is closed at  $t = 0$  sec then find out the value of-

- (a)  $I_L(0^-)$
- (b)  $V_C(0^-)$
- (c)  $I_R(0^+)$
- (d)  $I_C(0^+)$
- (e)  $V_C(0.2)$

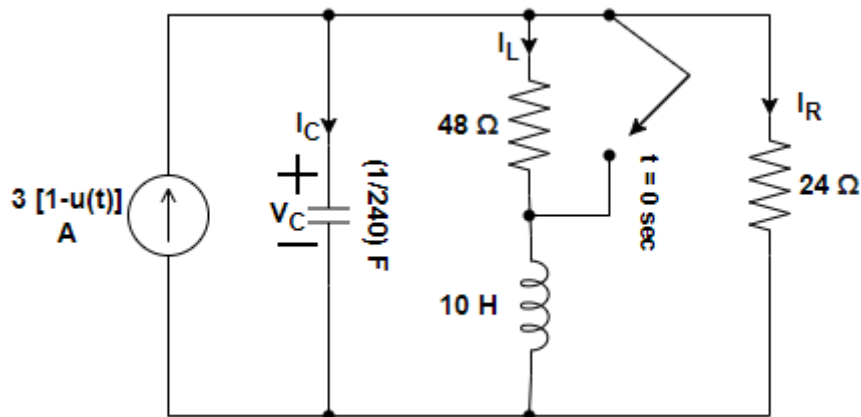


Figure 5

**Q6:** For the circuit of Figure-6, find the value of  $i(t)$  for  $t = \infty, 0^-, 0^+$  and  $100 \mu\text{sec}$ .

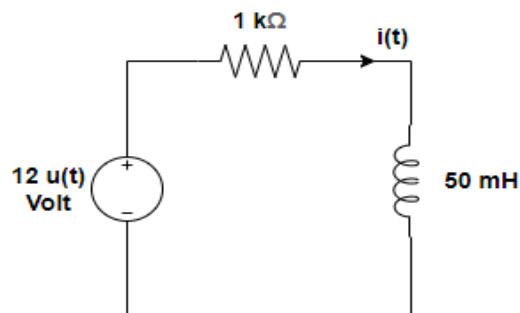


Figure 6

**Q7:** Determine the value and draw the curve of  $i(t)$  for all value of time in the circuit of Figure-7.

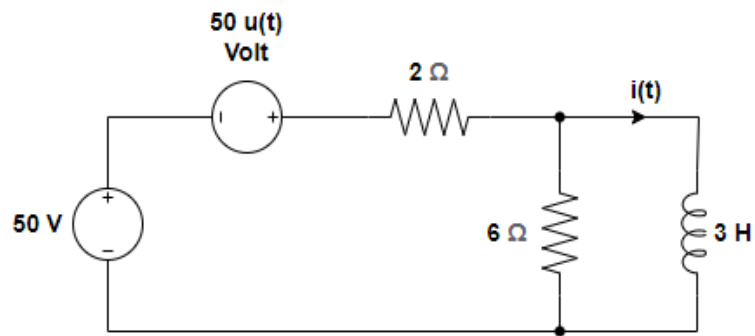


Figure 7

**Q8:** Find the capacitor voltage  $V_C(t)$  and the current  $i(t)$  in the  $200\ \Omega$  resistor of Figure-8 for all time. (The switch transfer from position **a** to **b** at time  $t=0$  sec).

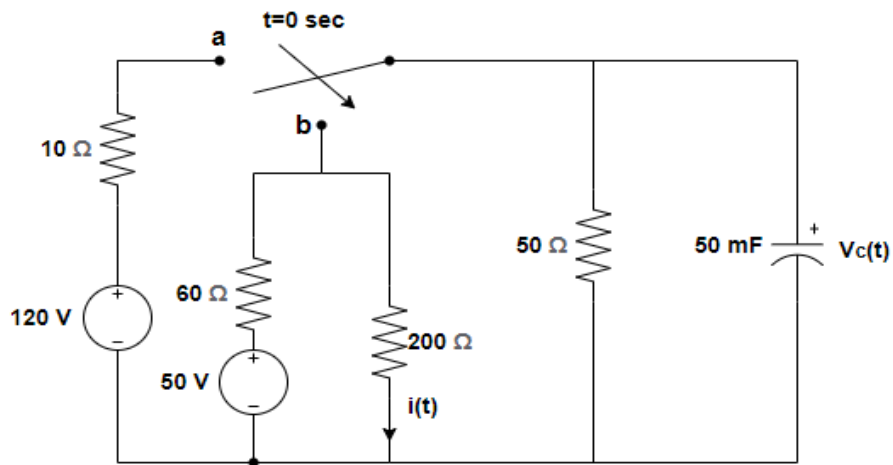


Figure 8