



# BE ASSIGNMENT-1

## SOLUTION

SOL (1) ÷

Case(I): circuit analysis at  $t=0^-$

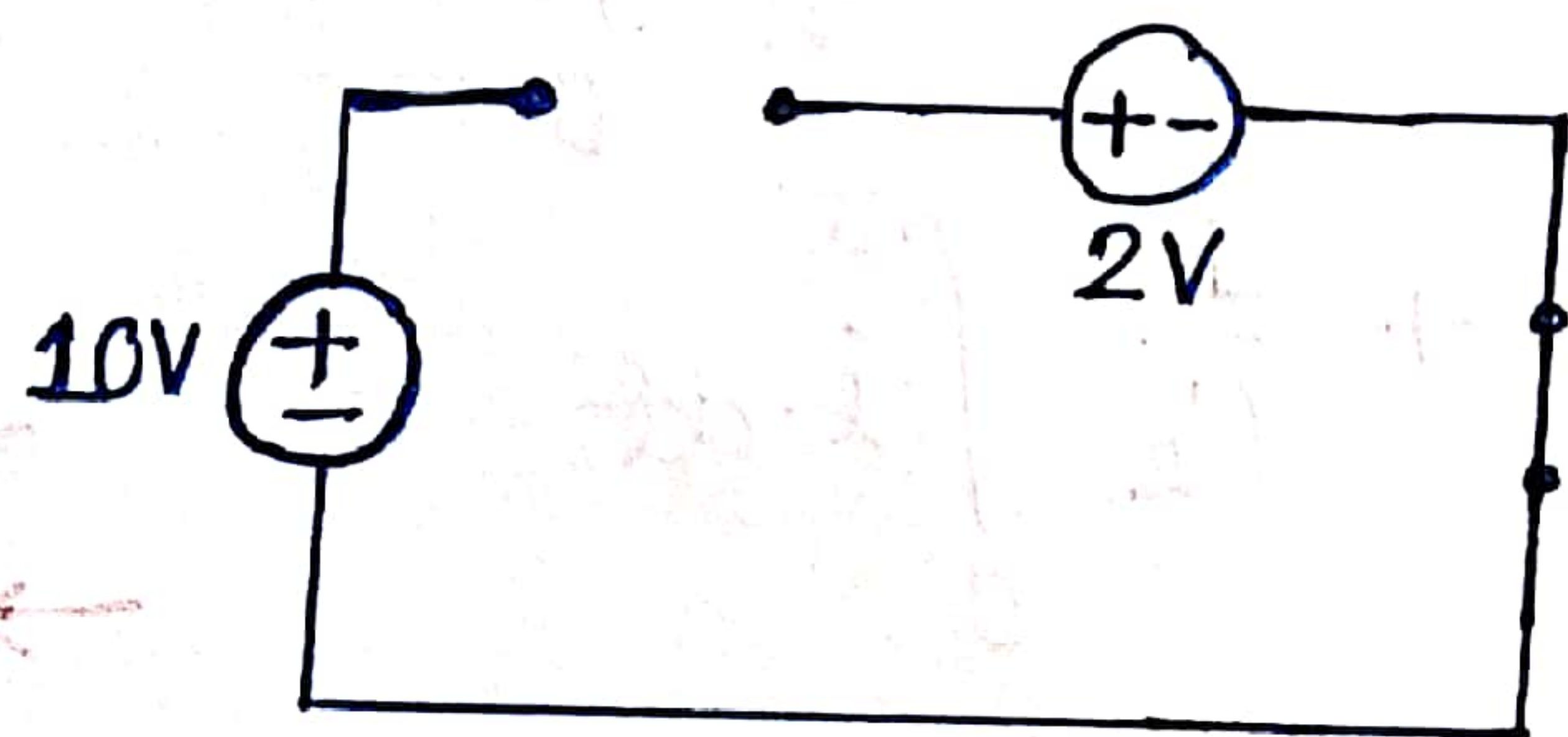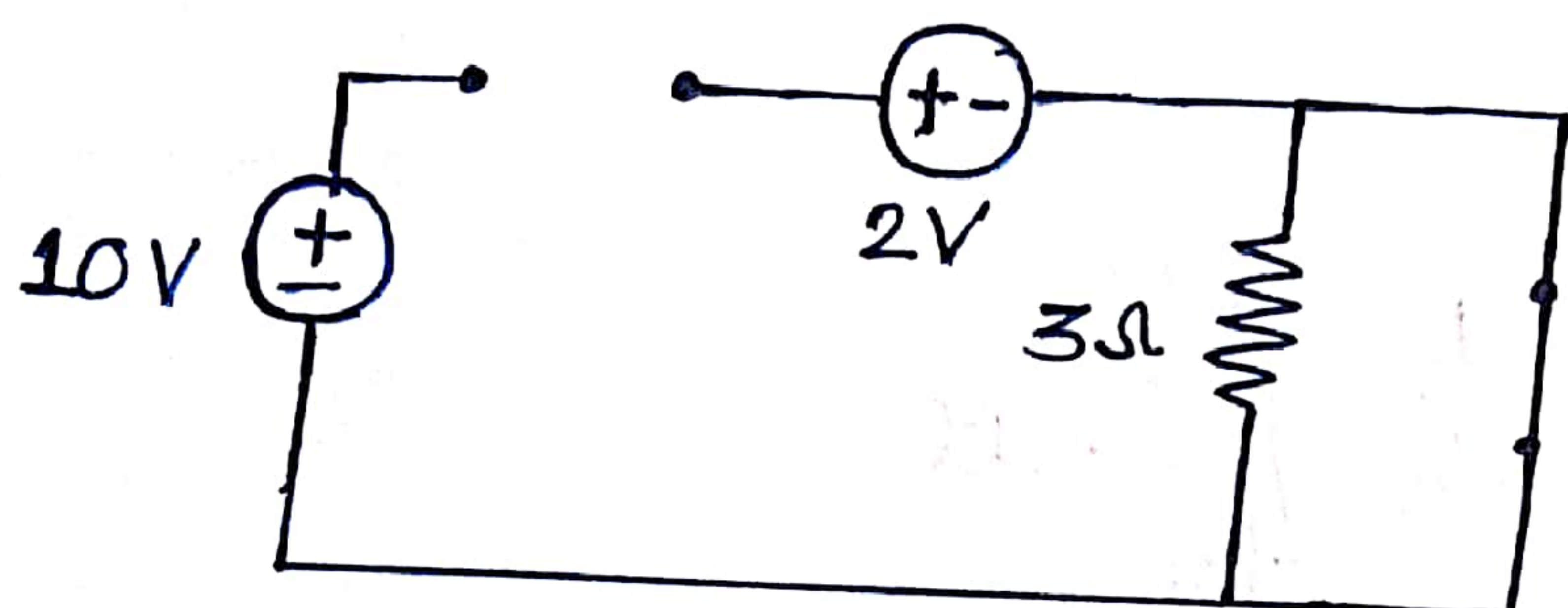Given that -  $V_{C_1}(0^-) = 2V$ ,  $V_{C_2}(0^-) = 0V$




Case(II): circuit analysis at  $t=0^+$


As we know that - capacitor does not allow sudden change of voltage. Hence -

$$V_{C_1}(0^+) = V_{C_1}(0^-) = 2V \quad \text{--- (1)}$$
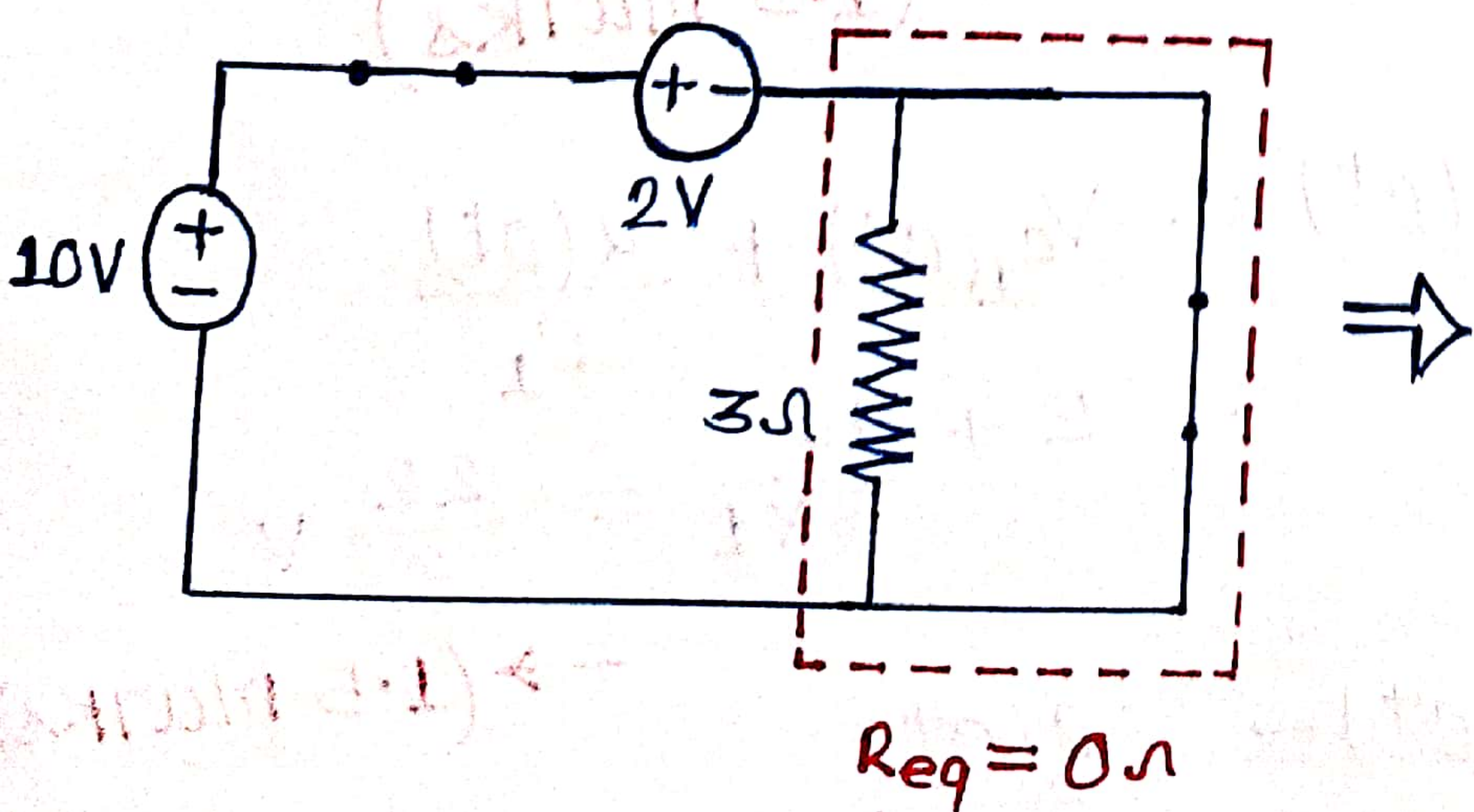
$$V_{C_2}(0^+) = V_{C_2}(0^-) = 0V \quad \text{--- (2)}$$




$$i = \frac{V_{eq}}{R_{eq}} = \infty$$

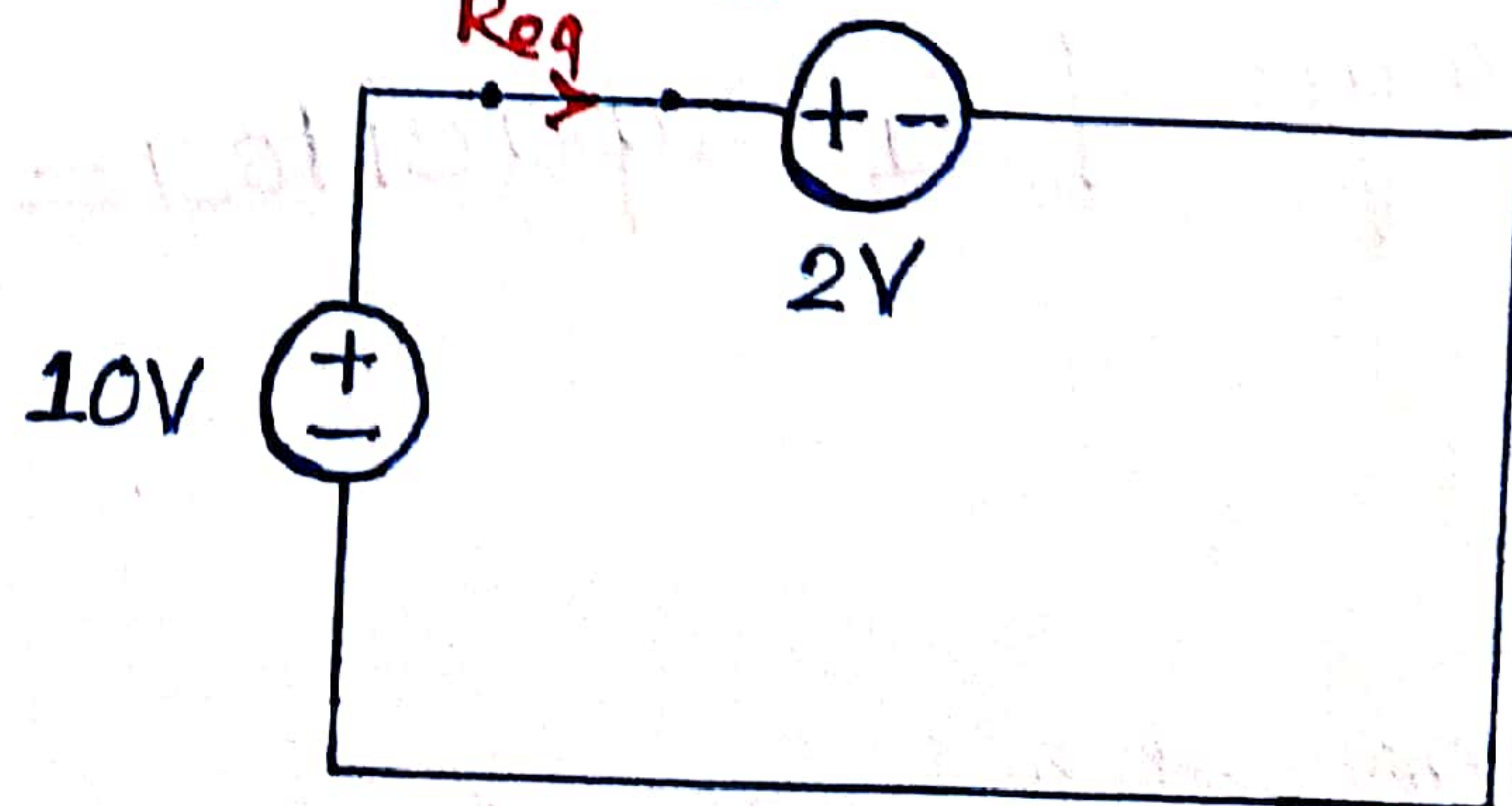

This circuit not satisfy KVL. Hence we can't use eq<sup>n</sup>(1) & eq<sup>n</sup>(2).

→ (1.5 Mark)



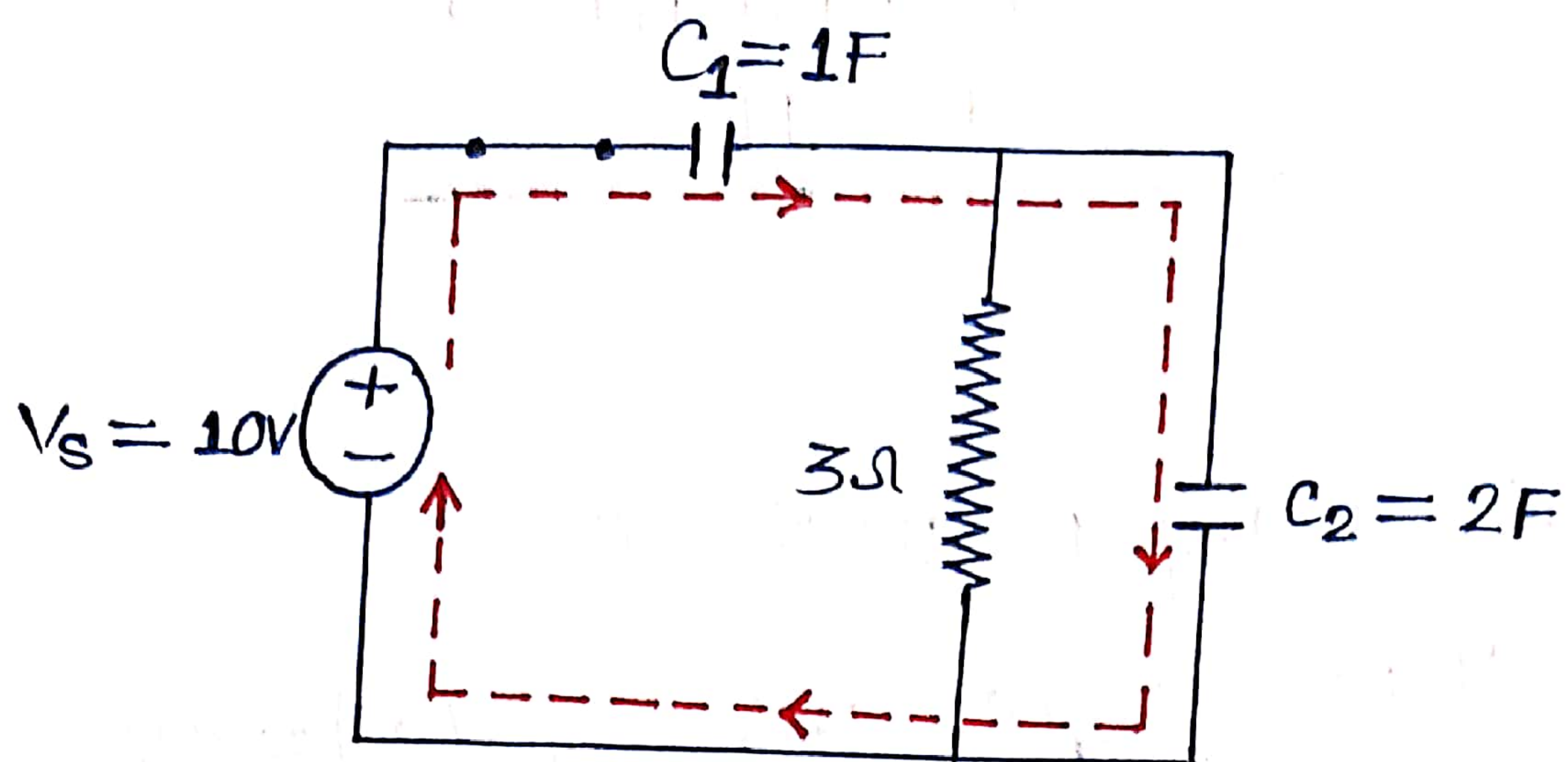

Apply KVL at the loop-

$$V_s = \frac{1}{C_1} \int_{-\infty}^t i \cdot dt + \frac{1}{C_2} \int_0^t i \cdot dt$$

$$V_s = \frac{1}{C_1} \int_{-\infty}^0 i \cdot dt + \frac{1}{C_1} \int_0^t i \cdot dt + \frac{1}{C_2} \int_0^t i \cdot dt$$

$$V_s = V_{C_1}(0^-) + \frac{1}{C_1} \int_0^t i \cdot dt + \frac{1}{C_2} \int_0^t i \cdot dt \quad \text{--- (3)}$$

→ (1.5 MARK)

Now put  $t = 0^+$  in eq<sup>n</sup> (3), we get -

$$V_s = V_{C_1}(0^-) + \frac{1}{C_1} \int_0^{0^+} i \cdot dt + \frac{1}{C_2} \int_0^{0^+} i \cdot dt$$

$$10 = 2 + \frac{Q(0^+)}{C_1} + \frac{Q(0^+)}{C_2}$$

$$8 = \frac{Q(0^+)}{1} + \frac{Q(0^+)}{2}$$

$$Q(0^+) = \frac{16}{3} \text{ C}$$

--- (4)

$$\left\{ \begin{array}{l} \frac{dQ}{dt} = i \\ Q = \int i \cdot dt \end{array} \right.$$

→ (1.5 MARKS)

$$\begin{aligned} \therefore \text{Voltage of } C_1 \text{ capacitor} &= V_{C_1}(0^+) = V_{C_1}(0^-) + \frac{Q(0^+)}{C_1} \\ &= 2 + \frac{16}{3 \times 1} = \frac{22}{3} \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore \text{Voltage of } C_2 \text{ capacitor} &= V_{C_2}(0^+) = \frac{Q(0^+)}{C_2} \\ &= \frac{16}{3 \times 2} = \frac{8}{3} \text{ V} \end{aligned}$$


→ (1.5 MARKS)



SOL(2):

Step(I): To calculate equivalent resistance between P & Q

$R = 300\Omega$

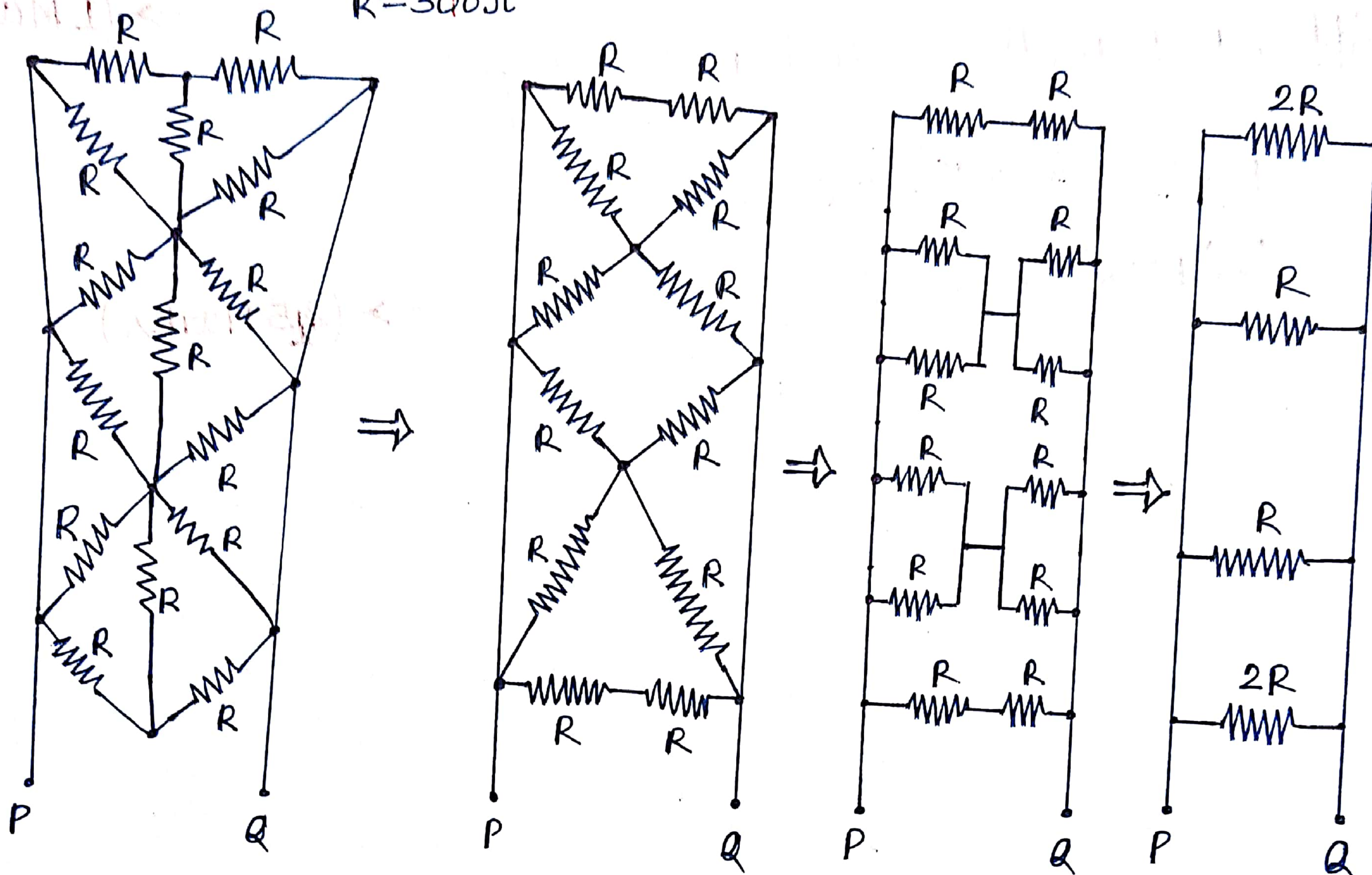



$\therefore$  Equivalent resistance between P & Q =  $R_{PQ}$

$$= \left( \frac{1}{2R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{2R} \right)^{-1}$$

$$= \frac{R}{3} = \frac{300}{3} = 100\Omega$$

$\rightarrow$  (3 MARKS)

Step(II):

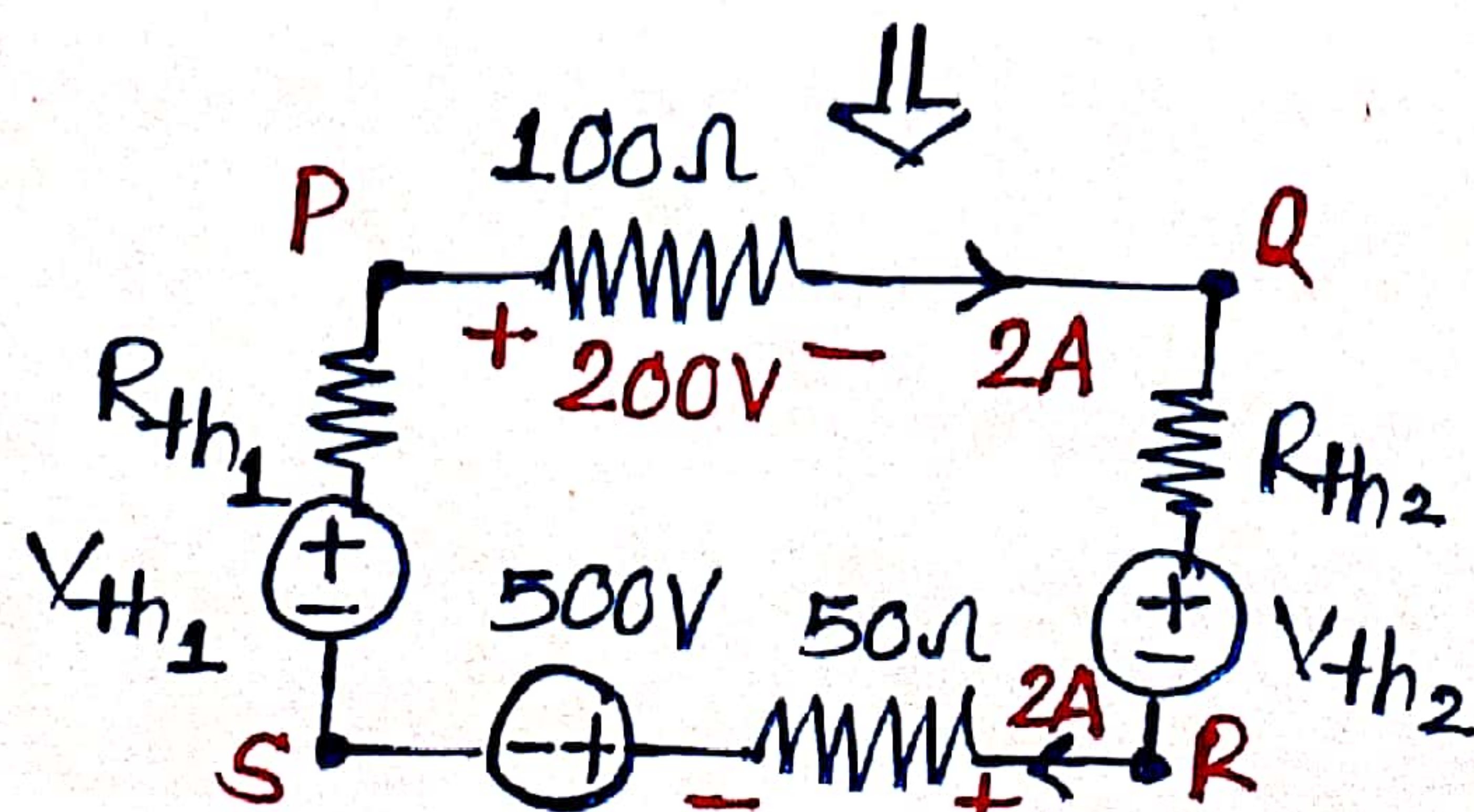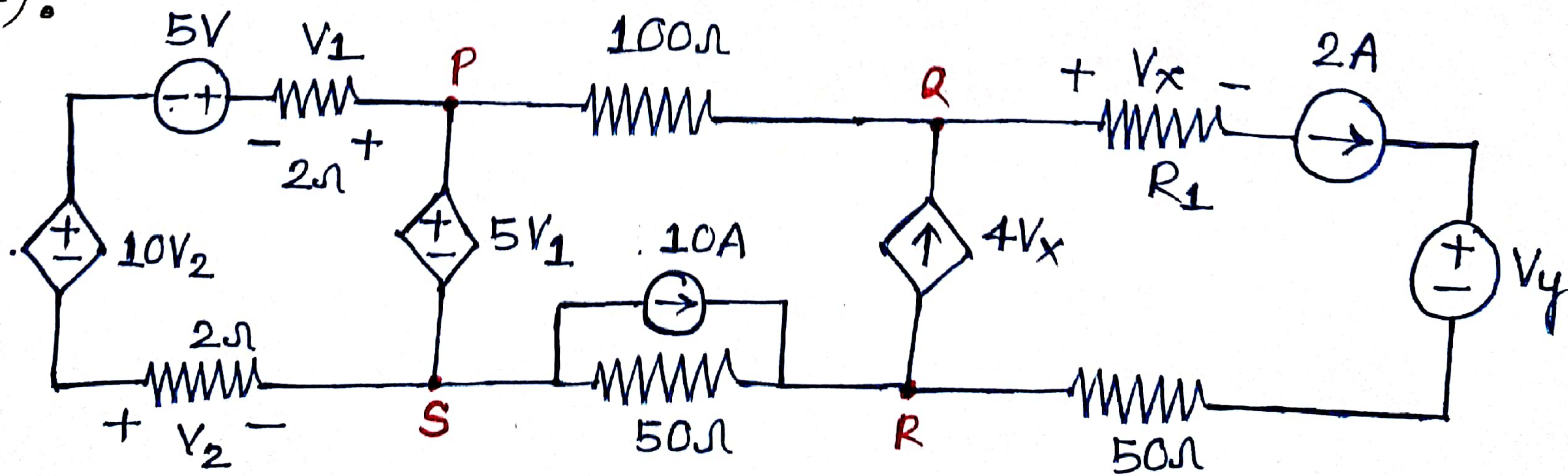



Current through  $100\Omega$  resistance  $= \frac{V_p - V_q}{100} = \frac{200}{100} = 2A$   $\rightarrow$  (1 Mark)

$\therefore$  Current through  $50\Omega$  resistance will also be  $2A$ .  $\rightarrow$  (1 Mark)


Apply KVL in the branch R-S, we get -

$$-V_R + 500 + 50 \times 2 + V_S = 0$$

$$\therefore (V_R - V_S) = 600V$$

$\rightarrow$  (2.5 Marks)



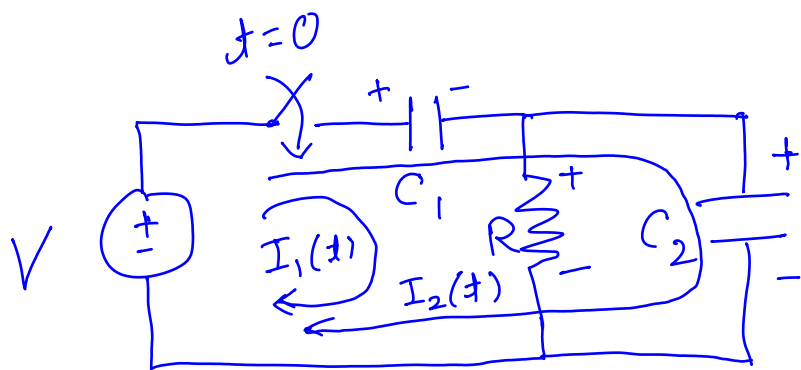

$$V_{C_1}(0^-) = V_0$$

$$V_{C_2}(0^-) = 0$$

$I_1(t)$ ,  $I_2(t)$  are loop currents.

KVL for the loop having  $I_1$  current

$$V = V_{C_1}(t) + V_R(t), \quad \forall t \geq 0 \quad (1)$$

KVL for the loop having  $I_2$  current

$$V = V_{C_1}(t) + V_{C_2}(t), \quad \forall t \geq 0 \quad (11)$$

Now

$$V_{C_1}(t) = V_{C_1}(0^-) + \frac{1}{C_1} \int_{0^-}^t I_{C_1}(\tau) d\tau$$

$$V_{C_2}(t) = V_{C_2}(0^-) + \frac{1}{C_2} \int_{0^-}^t I_{C_2}(\tau) d\tau$$

$$I_{C_1}(t) = I_1(t) + I_2(t)$$

$$I_{C_2}(t) = I_2(t), \quad V_R(t) = I_1(t)R$$

⊗ ⊗ since  $V$  (the source voltage) and  $V_0$  (the initial voltage of capacitor  $C_1$ ) are finite constants, we can infer all the branch voltages are finite for all time.

Hence  $I_1(t) = \frac{V_R(t)}{R}$  is also finite for all time.

From eq. (II),

$$\begin{aligned}
 V &= V_{C_1}(0^+) + V_{C_2}(0^+) \\
 &= V_{C_1}(0^-) + \frac{1}{C_1} \int_{0^-}^{0^+} (I_1(\tau) + I_2(\tau)) d\tau \\
 &\quad + V_{C_2}(0^-) + \frac{1}{C_2} \int_{0^-}^{0^+} I_2(\tau) d\tau \\
 &= V_0 + \frac{1}{C_1} \int_{0^-}^{0^+} I_2(\tau) d\tau + \frac{1}{C_2} \int_{0^-}^{0^+} I_2(\tau) d\tau
 \end{aligned}$$

Since  $\int_{0^-}^{0^+} I_1(\tau) d\tau = 0$  due to  $I_1(t)$  being finite at  $t=0$

$$\text{So, } V = V_0 + \frac{1}{C_1} q(0^+) + \frac{1}{C_2} q(0^+)$$

$$\text{where } q(0^+) \triangleq \int_{0^-}^{0^+} I_2(\tau) d\tau$$

$$\Rightarrow \left( \frac{1}{C_1} + \frac{1}{C_2} \right) q(0^+) = V - V_0$$

$$q(0^+) = \frac{C_1 C_2 (V - V_0)}{C_1 + C_2}$$

$$V_{C_1}(0^+) = V_{C_1}(0^-) + \frac{1}{C_1} q(0^+)$$

$$= V_0 + \frac{C_2 (V - V_0)}{C_1 + C_2}$$

$$= \frac{C_1 V_0 + C_2 V}{C_1 + C_2}$$

$$V_{C_2}(0^+) = \frac{1}{C_2} q(0^+) = \frac{C_1 (V - V_0)}{C_1 + C_2}$$

In the given problem,

$$V = 10V, \quad V_0 = 2V$$

$$C_1 = 1F, \quad C_2 = 2F$$

$$\Rightarrow V_{C_1}(0^+) = \frac{C_1 V_0 + C_2 V}{C_1 + C_2} = \frac{2 + 20}{3} V$$

$$= \frac{22}{3} V$$

$$V_{C_2}(0^+) = \frac{C_1(V - V_0)}{C_1 + C_2} = \frac{8}{3} V$$



