

CSE 112: Computer Organization

Instructor: Sujay Deb

Lecture 11



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



Single-Cycle RISC-V Processor

Example Program

- Design datapath
- View example program executing

Example Program:


Address	Instruction	Type	Fields					Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op	0000011	FFC4A303
0x1004	sw x6, 8(x9)	S	imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	0100011 0064A423
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	0110011 0062E233
0x100C	beq x4, x4, L7	B	imm _{12,10:5}	rs2	rs1	f3	imm _{4:1,11}	op	1100011 FE420AE3

Single-Cycle RISC-V Processor

- **Datapath:** start with `lw` instruction


- **Example:** `lw x6, -4(x9)`
`lw rd, imm(rs1)`

I-Type

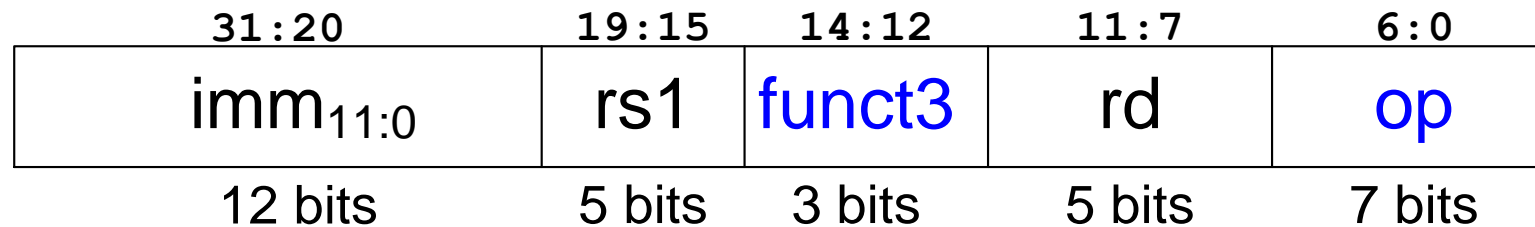


Single-Cycle Datapath: lw fetch

STEP 1: Fetch instruction

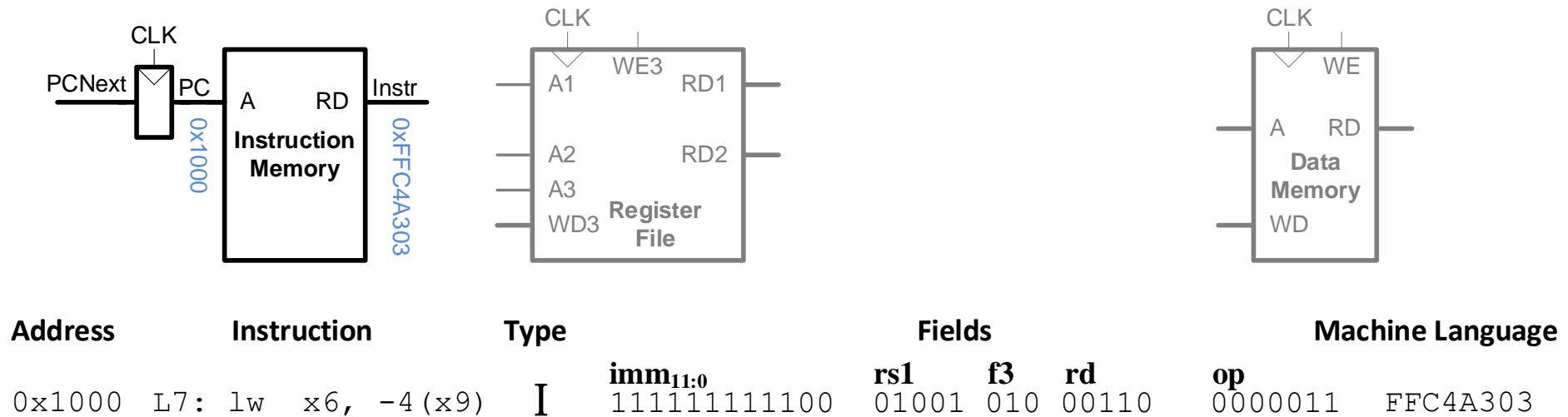


Single-Cycle Datapath: lw Reg Read

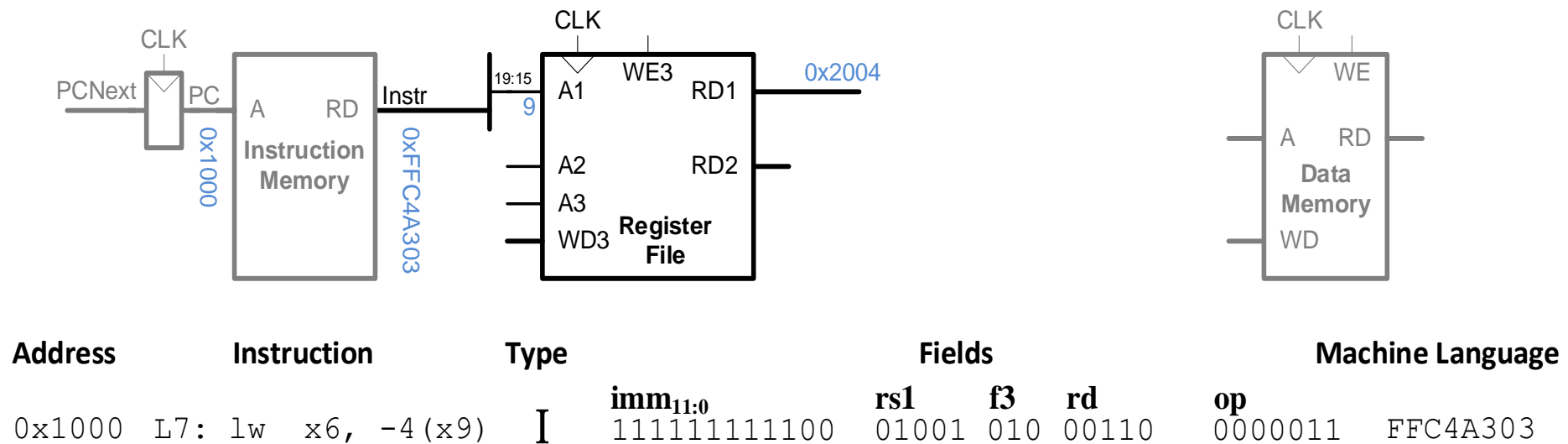STEP 2: Read source operand (**rs1**) from RF




Single-Cycle Datapath: lw Immediate

STEP 3: Extend the immediate

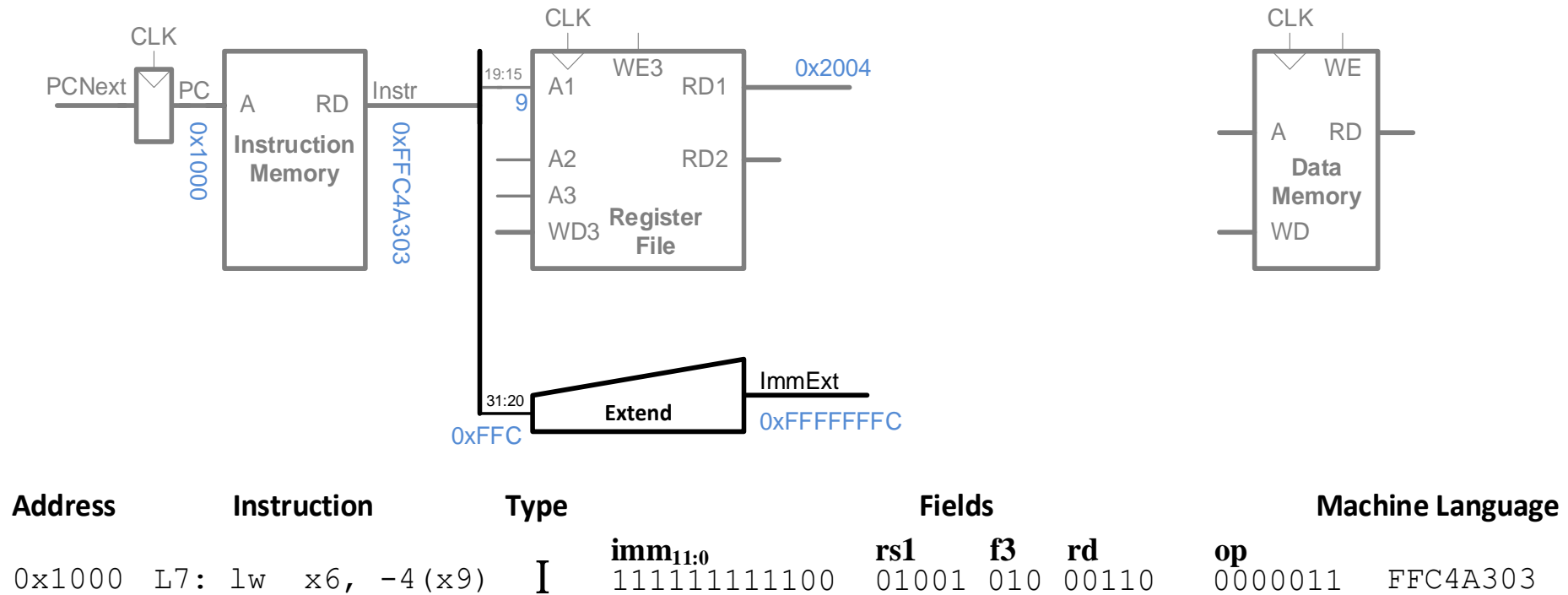

Single-Cycle Datapath: lw Address

STEP 4: Compute the memory address

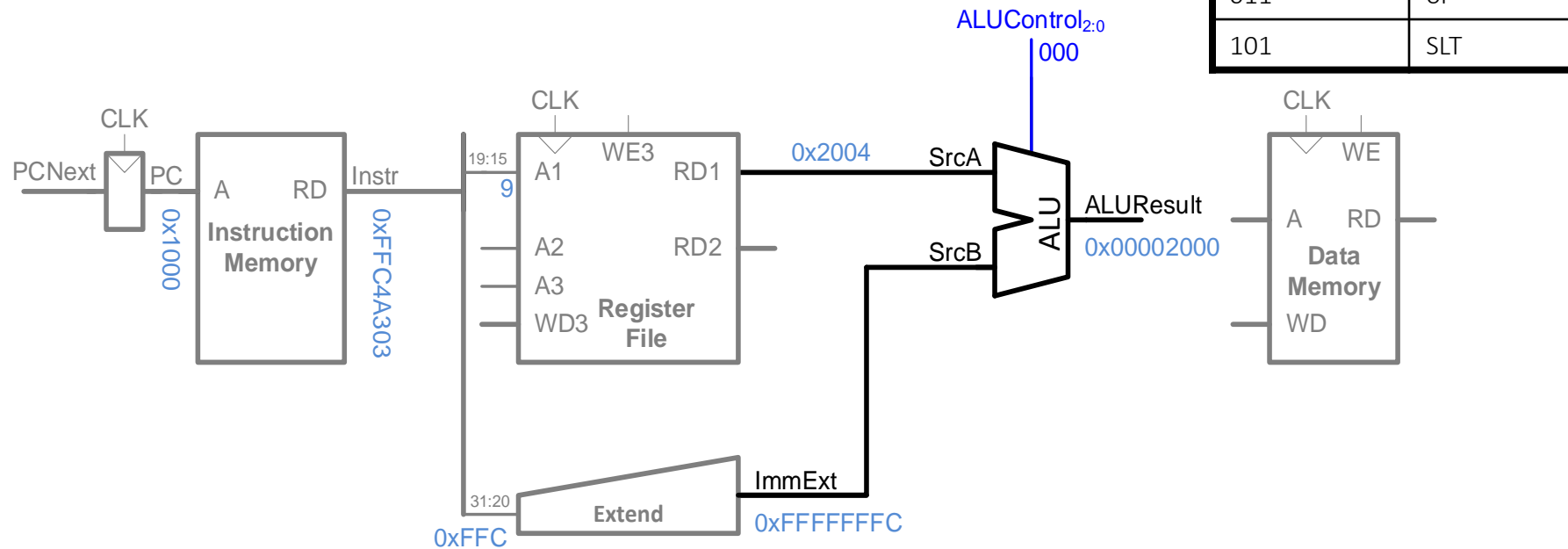


ALUControl _{2,0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm_{11:0} 111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303

Single-Cycle Datapath: lw Mem Read

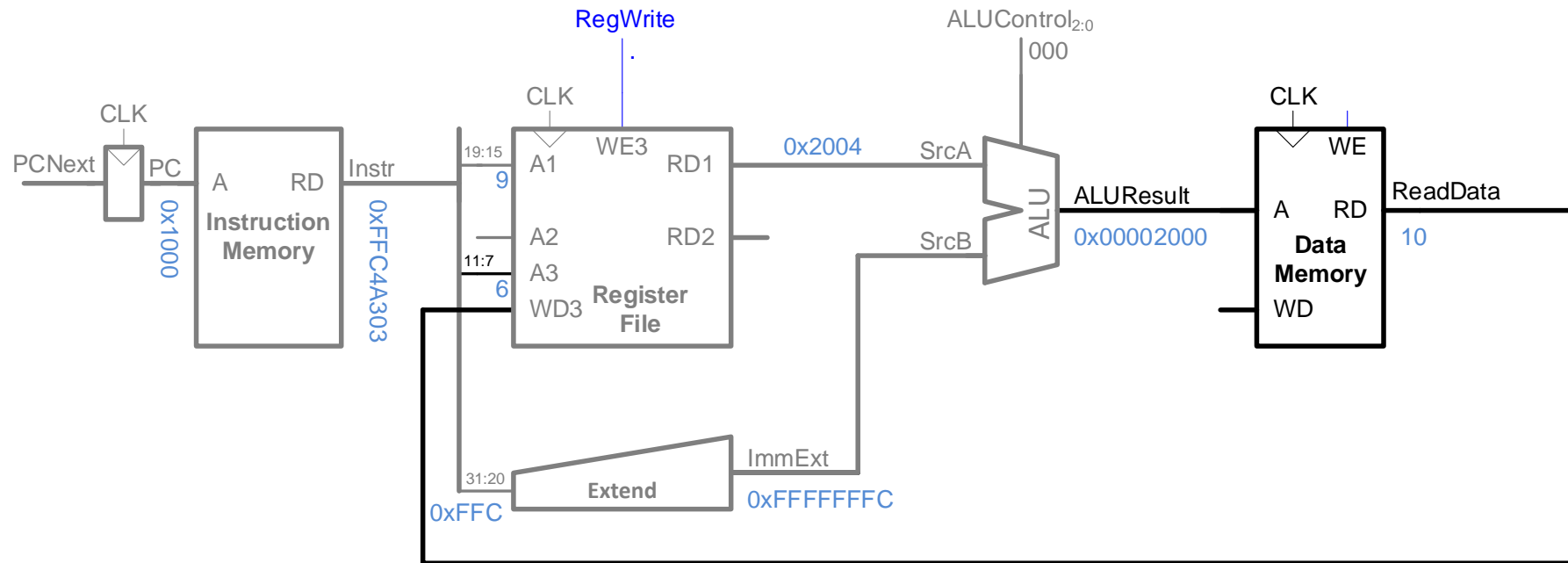
STEP 5: Read data from memory and write it back to register file



Address	Instruction	Type	Fields	Machine Language										
0x1000	L7: lw x6, -4(x9)	I	<table><tr><th>imm_{11:0}</th><th>rs1</th><th>f3</th><th>rd</th><th>op</th></tr><tr><td>111111111100</td><td>01001</td><td>010</td><td>00110</td><td>0000011</td></tr></table>	imm _{11:0}	rs1	f3	rd	op	111111111100	01001	010	00110	0000011	FFC4A303
imm _{11:0}	rs1	f3	rd	op										
111111111100	01001	010	00110	0000011										

Single-Cycle Datapath: PC Increment

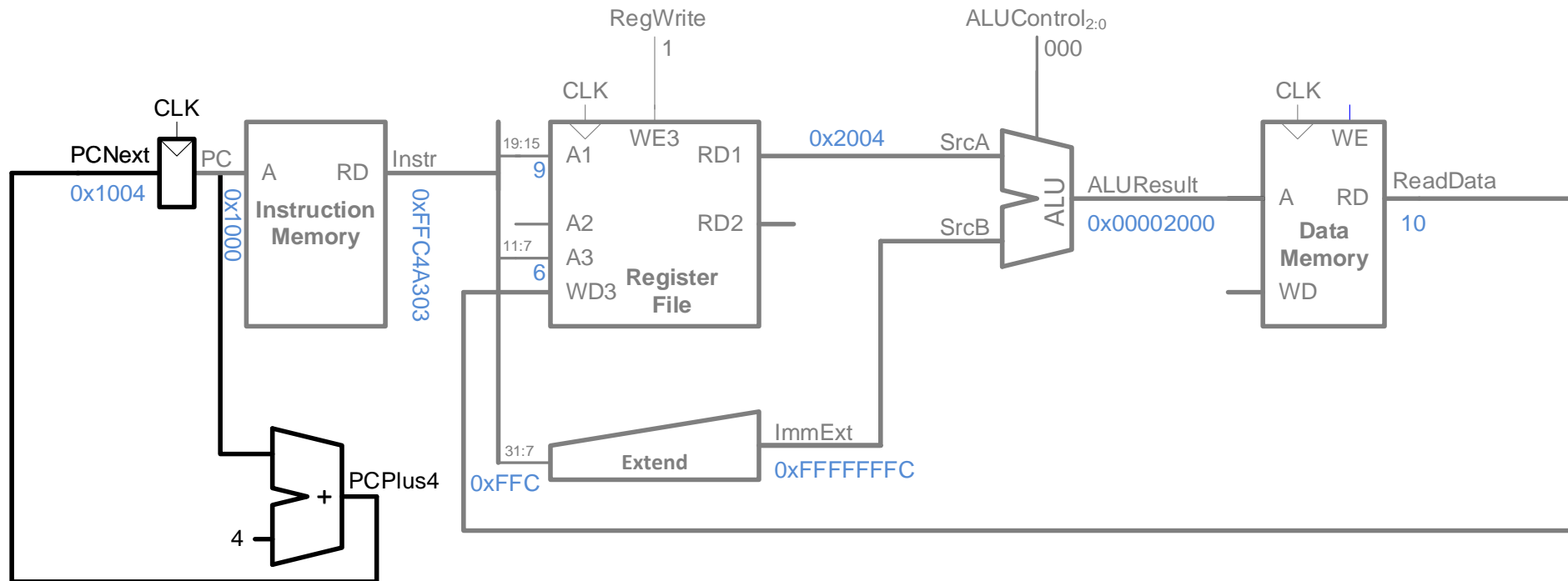STEP 6: Determine address of next instruction




Address	Instruction	Type	Fields			Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op
			111111111100	01001	010	00110	0000011
							FFC4A303

Single-Cycle Datapath: Other Instructions

Single-Cycle Datapath: sw

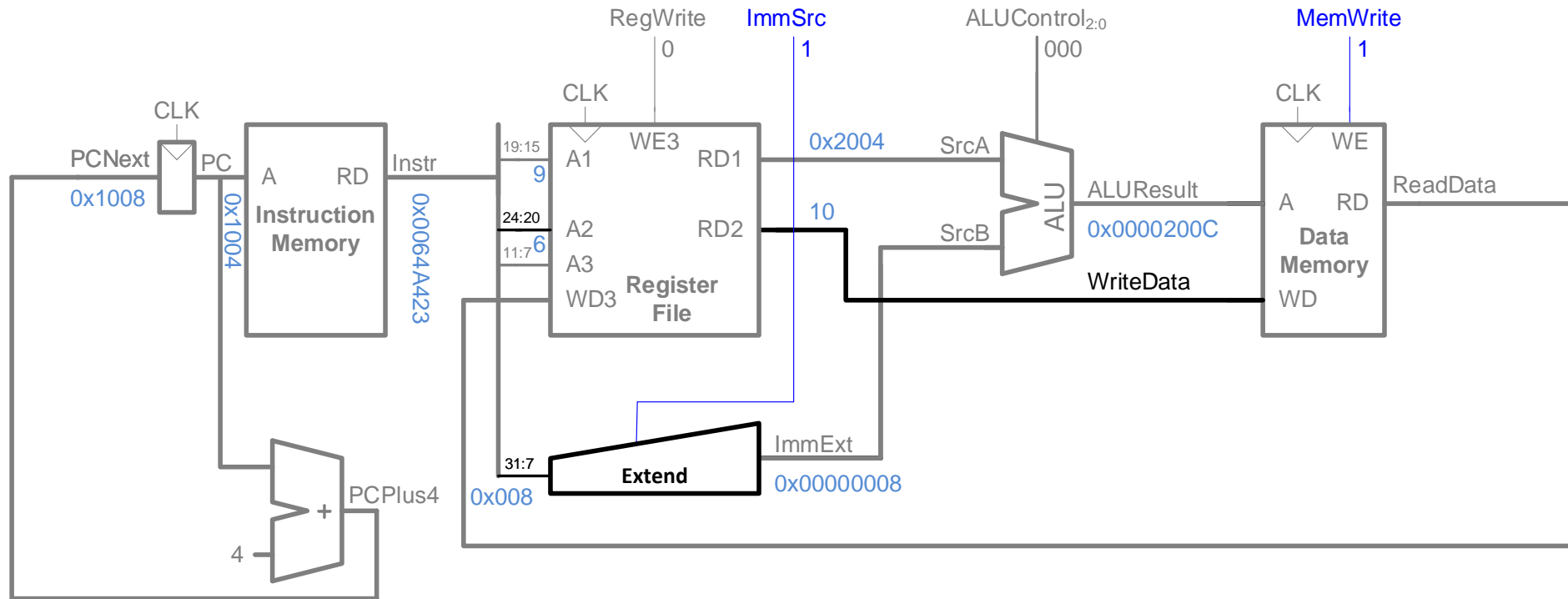- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite




Address	Instruction	Type	Fields					Machine Language	
0x1004	sw x6, 8(x9)	S	imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	0064A423
			00000000	00110	01001	010	01000	0100011	


Single-Cycle Datapath: Immediate

ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, instr[31:20] }	I-Type
1	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type

I-Type

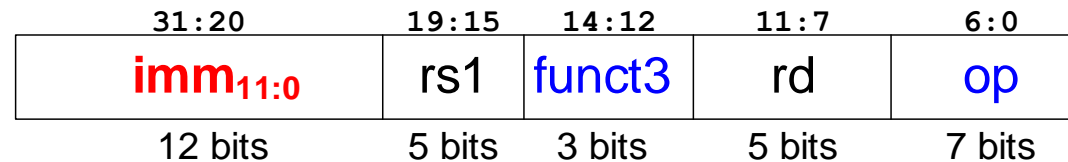


S-Type

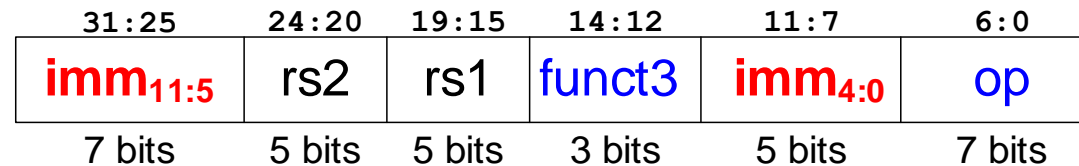

Single-Cycle Datapath: R-type

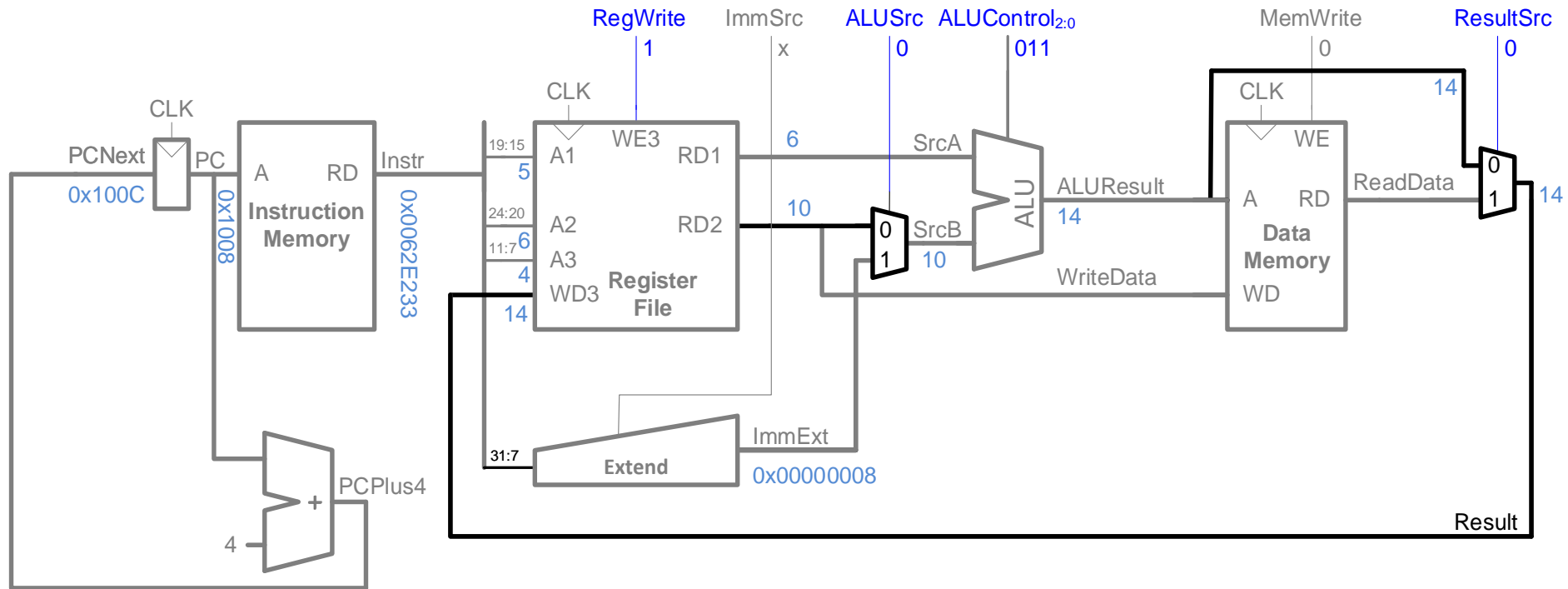
- Read from **rs1** and **rs2** (instead of imm)
- Write *ALUResult* to **rd**



Address	Instruction	Type	Fields					Machine Language	
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	0062E233
			0000000	00110	00101	110	00100	0110011	

Single-Cycle Datapath: beq

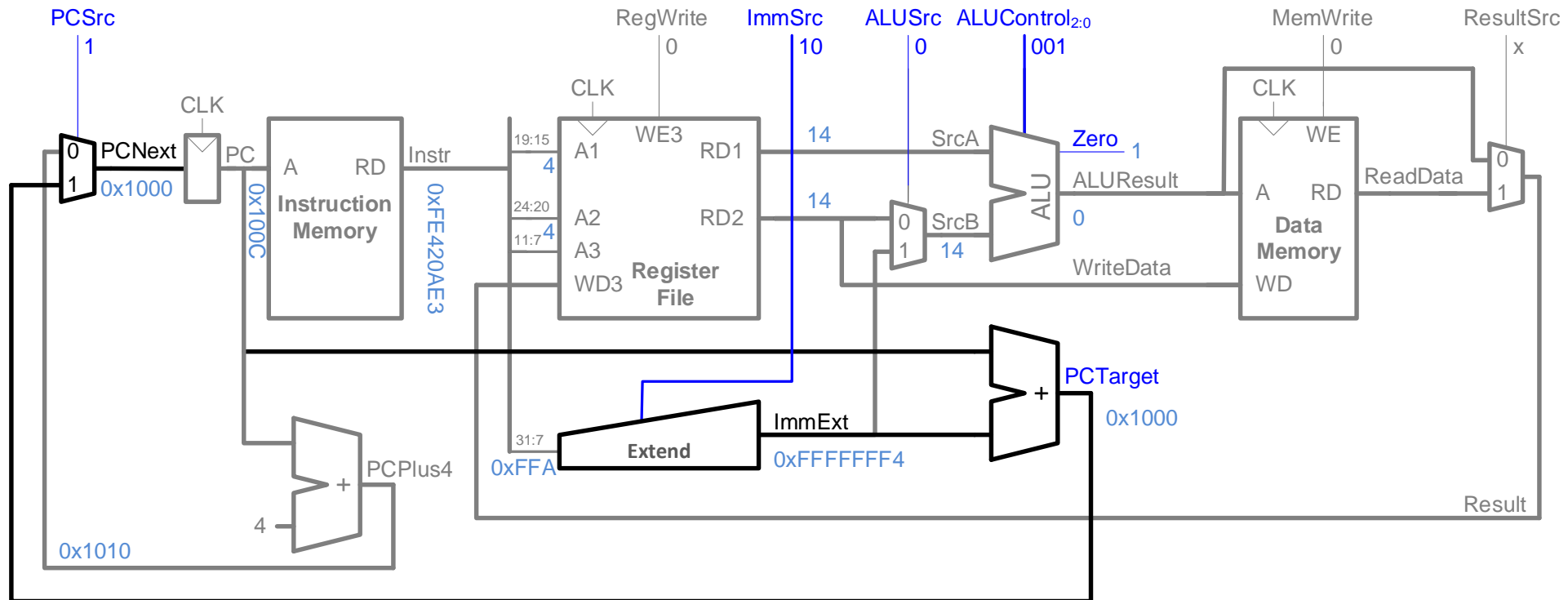Calculate **target address**: $PCTarget = PC + imm$




Address	Instruction	Type	Fields						Machine Language
			imm_{12,10:5}	rs2	rs1	f3	imm_{4:1,11}	op	
0x100C	beq x4, x4, L7	B	1111111	00100	00100	000	10101	1100011	FE420AE3


Single-Cycle Datapath: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20] }	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0 }	B-Type


I-Type

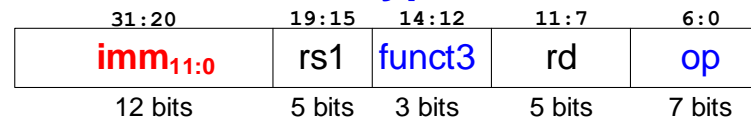


S-Type

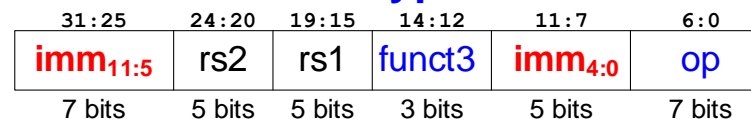

B-Type

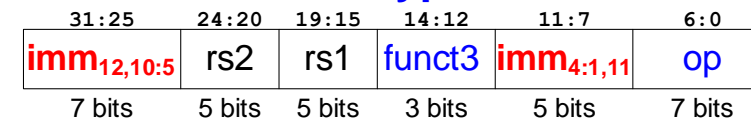


Single-Cycle RISC-V Processor

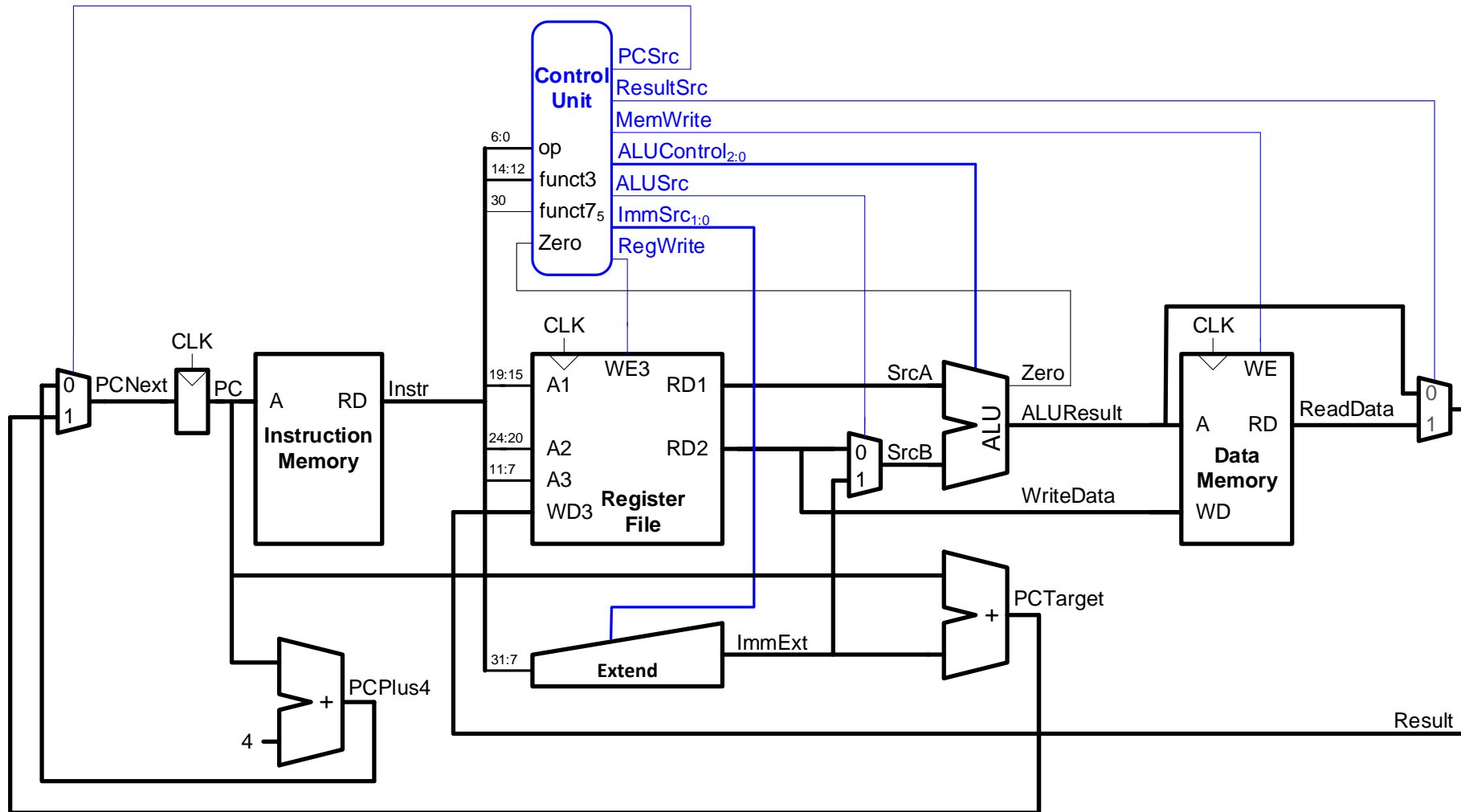


Single-Cycle Control

Single-Cycle Control

High-Level View

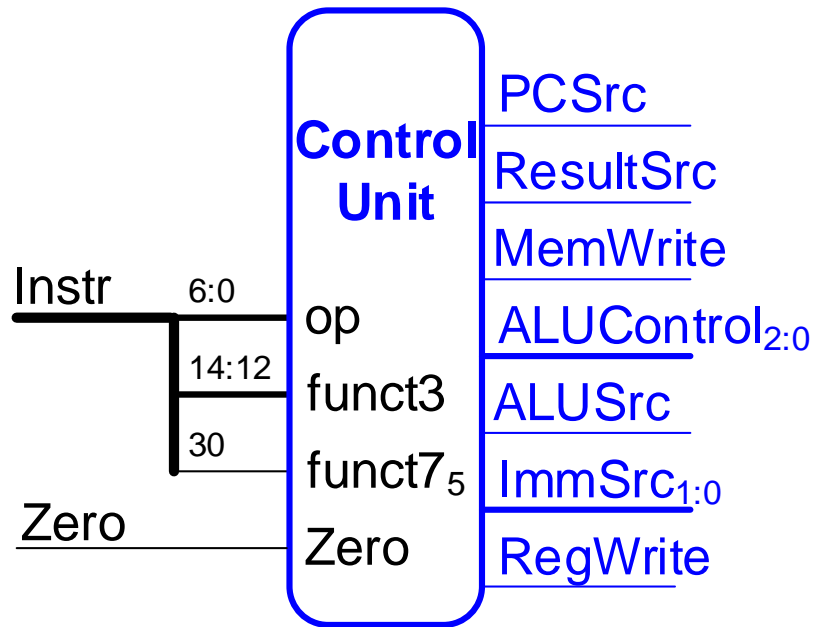


Low-Level View

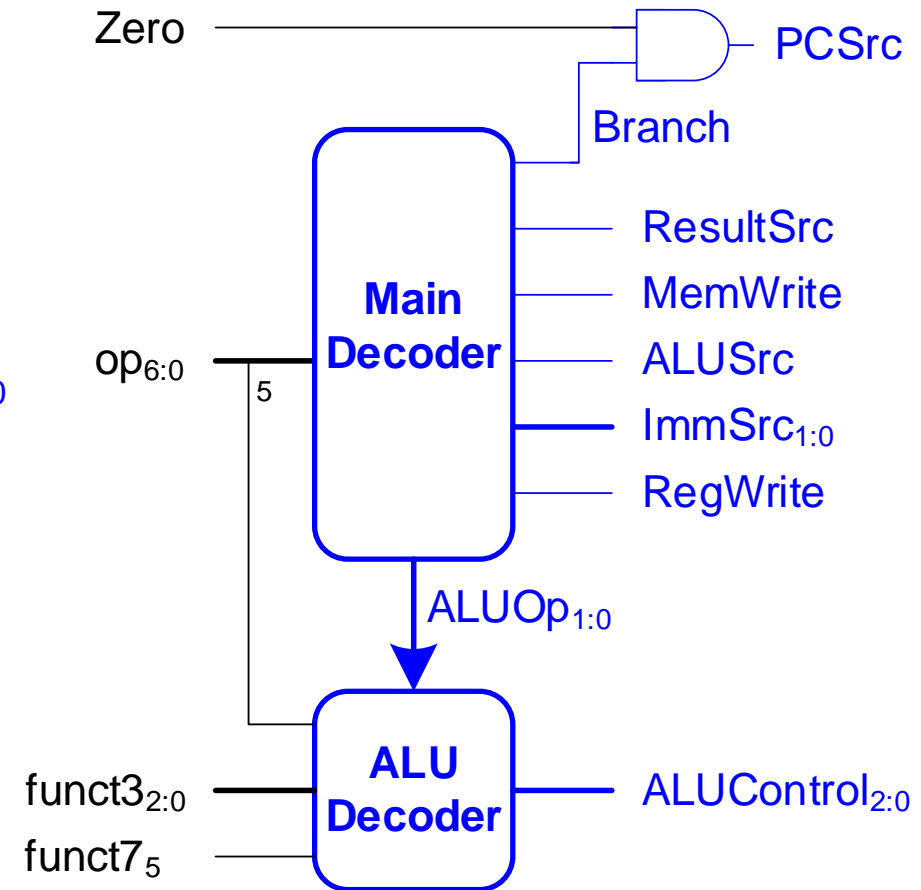

Single-Cycle Control: Main Decoder

op	Instr.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw							
35	sw							
51	R-type							
99	beq							

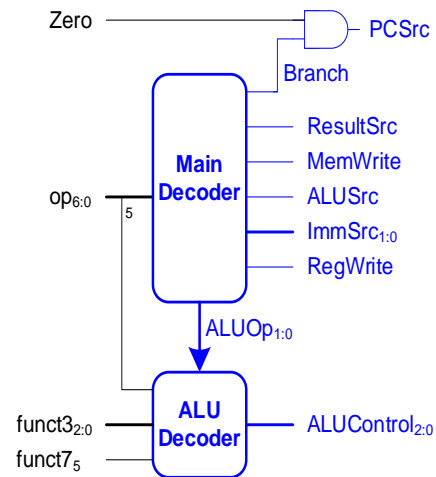


Class Interaction # 13



Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

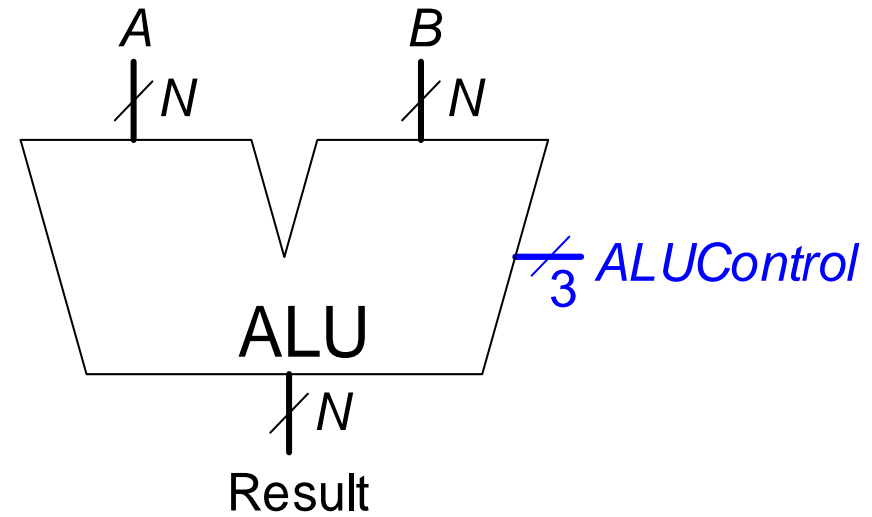

Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

